## **Course Outline**

- 1. Introduction to WECC
- 2. Fundamentals of Electricity
- 3. Power System Overview
- 4. Principles of Generation
- 5. Substation Overview
- 6. Transformers
- 7. Power Transmission
- 8. System Protection
- 9. Principles of System Operation

## 2 | Fundamentals of Electricity

- Electric Theory, Quantities and Circuit Elements
- Alternating Current
- Power in AC Circuits
- Three-Phase Circuits
- Electromechanics

## Charge, Force and Voltage



- Atoms, Electrons, Charge
- Conductors and Insulators
- Current
- Voltage
- Power
- Magnetism and Electromagnetism
- Circuit Components and Resistance
- Circuit Analysis (Ohm's and Kirchoff's Laws)


## Electric Theory, Quantities and Circuit Elements Electricity

- Electricity is the set of <u>physical</u> phenomena associated with the presence and flow of <u>electric charge</u>. Including:
- Lightning and Static electricity
- <u>Electromagnetic induction</u>
- <u>Current</u>
- Electromagnetic radiation and radio waves
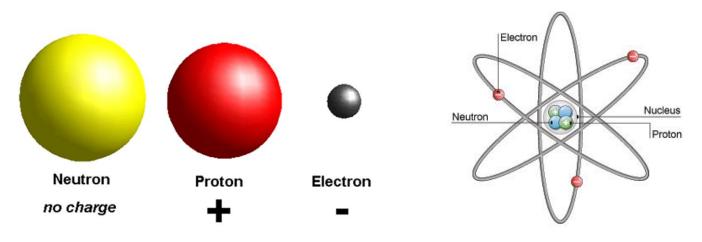
## Atoms, Electrons, Charge

7

- Matter has weight and occupies space.
- Matter is composed of atoms.




- Atoms are composed of:
  - Electrons(-) orbiting around a nucleus of Protons(+) and Neutrons.

Electrons have a negative charge Protons have a positive charge **Opposite charges attract** Like charges repel Field = 0 Field = 0

An Electric (force) field surrounds any charged object – it spreads out - weakens with distance.

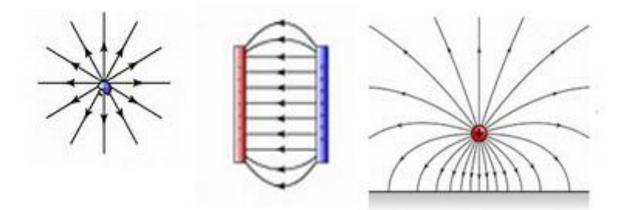
Electric field around various shaped objects




- Charge is measured in Coulombs
- 1 Coulomb =1 amp per second
- The charge of one electron is -1.6 X 10<sup>-19</sup> Coulombs.  $1 Coulomb = \frac{1}{-1.6 * 10^{-19}} = 6.25 * 10^{18} Electrons$

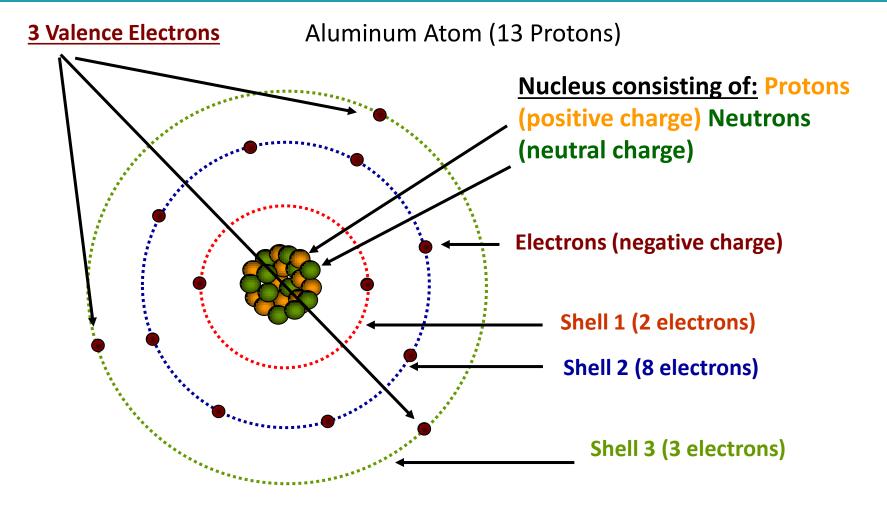
### 6,250,000,000,000,000,000 electrons!

- Electrons orbiting the nucleus are organized into <u>shells</u>
- The number of protons in an atom determine what the element is
- For instance:
  - Hydrogen 1 proton and 1 electron
  - Aluminum 13 protons and 13 electrons



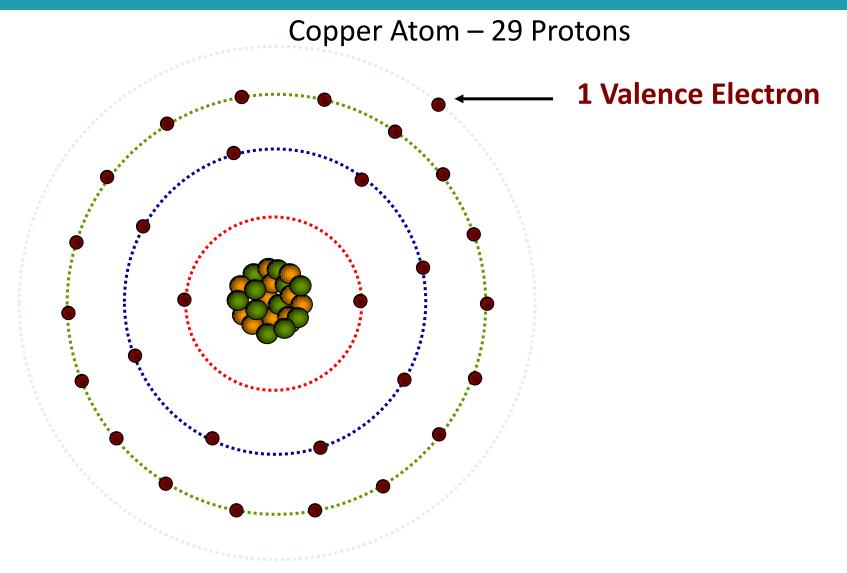

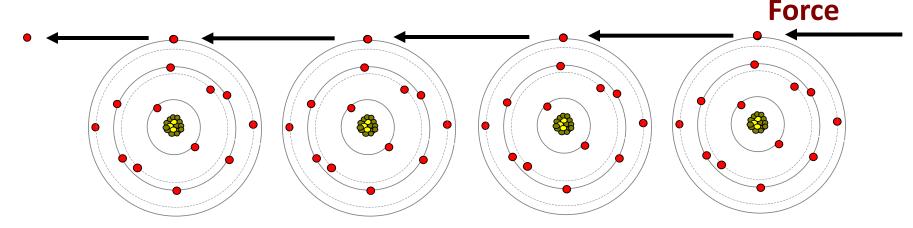- Free Electrons jump easily from one atom to another
- The number of shells, and electrons in each shell, determine how tightly they are bound to the atom
- In a good conductor the valence electrons can be easily forced to move from one atom to the next



An external force can cause the free electrons to move from one atom to the next.

friction (static), thermal (thermocouple), light (photocell), chemical (battery) or electromagnetic (generator)

## **Conductors and Insulators**

When it comes to electricity there are generally two types of material:

- -Conductors
- -Insulators






A *conductor* is a material that has a large number of free electrons that continually jump to other atoms.

 Good electrical conductors are copper and aluminum. Gold, silver, and platinum are also good conductors, but are very expensive

An *insulator* is a material that has only a few free electrons. In insulators, the electrons are tightly bound by the nucleus.

 Good electrical insulators are rubber, porcelain, glass, and dry wood

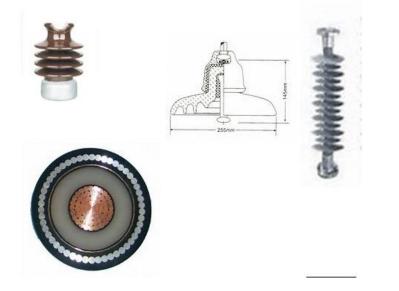- Insulators prevent current from flowing
- Insulators are used to isolate electrical components and prevent current flow





#### **Conductors and Insulators**

### **Insulator Characteristics**

**Resistance** - The ability of the insulator to resist current leakage through and over the surface of the insulator material.

**Dielectric Strength** - The ability to withstand a maximum voltage without breakdown damage to the insulator.

## Check Your Knowledge: Fundamentals of Electricity

- In general are objects charged, or neutral? Why is that?
- 2. Where do you see static electricity?
- 3. What are good conductors? What are good insulators?
- 4. What decides which conductor you should use?

## Current



**Current (I)** is the movement of charge through a conductor. Electrons carry the charge.

- Unit of measurement: Amperes (A)
- One ampere (amp) of current is one coulomb of charge passing a point on a conductor in one second
- This measurement is analogous to "gallons or liters per second" when measuring the flow of water

**Direct Current (DC)** flows in only one direction.

 Many uses including: Batteries, electronic circuits, LED lights, generator excitation systems and rotors, DC transmission lines – and much more

**Alternating Current (AC)** continuously changes in magnitude and direction.

- AC is used by most lights, appliances and motors. It is used in the high voltage transmission system
- AC enables use of transformers to change voltage from high to low and back

### **Typical Current Levels:**

Cell phone battery charger	5/1000 Amps = 5mA = (5 milli-amps)
Sensation	.25mA
Let-go threshold	5mA
Potentially lethal	50mA
40 watt incandescent light bulb	.33 Amps
Toaster	10 Amps
Car Starter Motor	100+ Amps
Transmission line conductor	1000 Amps
Lightning Bolt or Ground Fault	20,000+ Amps




# Voltage



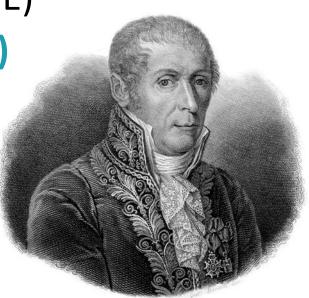
## Electric Theory, Quantities and Circuit Elements Voltage

- **Voltage (V)** is the force that causes electrons to move.
- Voltage is also referred to as potential difference or electromotive force (emf or E)
- Unit of measurement: Volts (V)
- Similar to "pounds per square inch" when measuring water pressure.




Alessandro Volta (1745–1827)
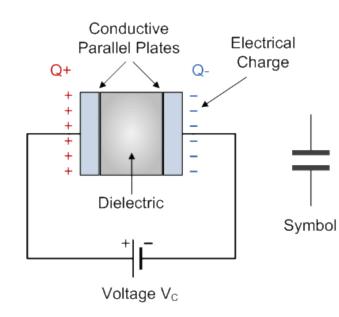
## Electric Theory, Quantities and Circuit Elements Voltage Sources





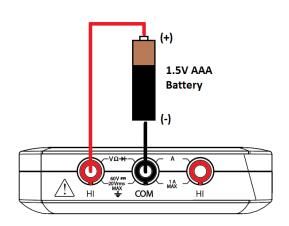


## Electric Theory, Quantities and Circuit Elements Voltage

#### Sample Voltage Levels


AA Battery	1.5v
Car Battery	12v
Household	120v
<b>Distribution Feeder Circuit</b>	12.47kV
High Voltage Line	47kV to 500kV
Lightning	1,000,000+ volts



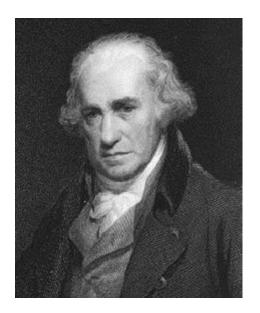- **Power (P)** is the *rate* at which work is being performed.
- Unit of Measurement: watts (w)
- Power = Voltage x Current
- This means that the electrical energy is being converted into another form of energy (e.g. heat energy, light energy, mechanical energy, etc.)



James Watt, 1736 -1819

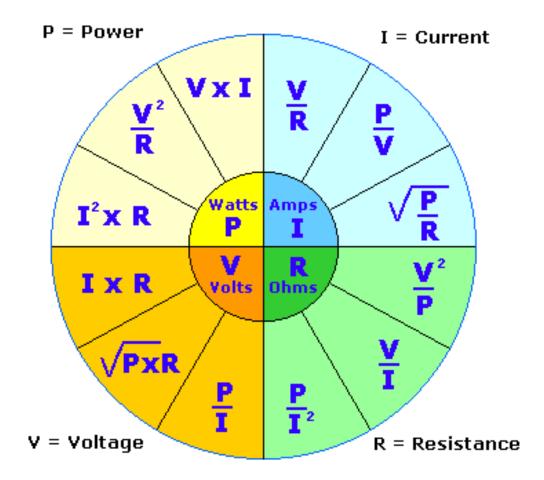

WESTERN ELECTRICITY COORDINATING COUNCIL

#### **Sample Power Calculation**

A Toaster uses 120-volts and allows 10 amps of current to flow. How much power does it consume?

**Instructions:** Using the formula for power and substituting the known values, we have:

$$P = VI$$

$$P = (\___)(\__)$$

$$P = \_$$



#### **Sample Power Calculation**

A Toaster uses 120-volts and allows 10 amps of current to flow. How much power does it consume?

**Instructions:** Using the formula for power and substituting the known values, we have:

$$P = VI$$
  

$$P = (120V)(10A)$$
  

$$P = 1200 Watts$$



• A "watt" is an instantaneous value, it is the power being used at any given instant of time

 A "watt hour" indicates how much power is being consumed over an hour

watt x time (in hours) = watt hours = energy

Retail Power consumption is typically measured in kilowatt hours (KWh)

Kilowatts x time (in hours) = Kilowatt hours

Example:

5,000 watts used for 3 hours

5,000 = 5 kW

5 kW x 3 hours = 15 kWh

Wholesale power consumption is typically measured in megawatt hours (MWh)

# Example Power Use:

- Small light bulb 40 watts
- Toaster 1000 watts or 1 kW
- Household 5–10kW
- One horsepower 746 watts (.746 kW)
- Wind turbine 1,000 kW or 1.0 MW
- Power Plant 500 MW

# Example Power Use:

Small light bulb	40 watts
Toaster	1000 watts or 1 kilowatt (1kW)
Household	5 – 10kW
One horsepower	746 watts (.746 kW)
Wind turbine	1,000 kW or 1.0 Megawatts (MW)
Combined Cycle Power Plant	500 MW


# Check Your Knowledge: Fundamentals of Electricity

- 1. How many volts does a hair dryer use?
- 2. How many amps?
- 3. How many watts?
- 4. How many watts are consumed in a city at 7:00am where 50,000 people are simultaneously drying their hair to get ready for work?
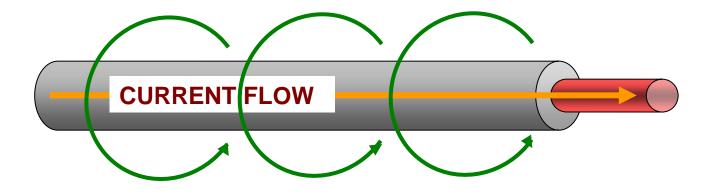
# Magnetism and Electromagnetism

Wherever an electric current exists, a *magnetic field* also exists.

- The magnetic field carries the invisible force of magnetism
- The magnetic field surrounds the conductor



Whenever current flows through a conductor, a *magnetic field* is created around the conductor.

# What happens when you drop a magnet in a copper tube?

С

W

F

N

TRICI


С

O O R D I N A T

G

N


Социс

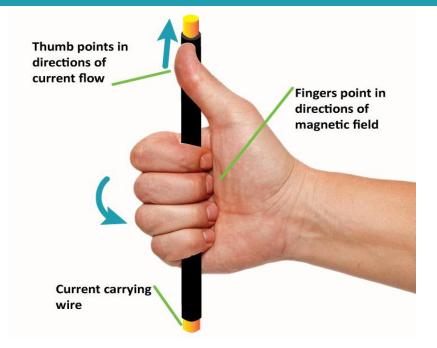


#### *Right hand rule* for <u>Magnetic Field</u> around a conductor.


Assumes Current flows from Positive to Negative

#### **Magnetic Field Lines of Force**

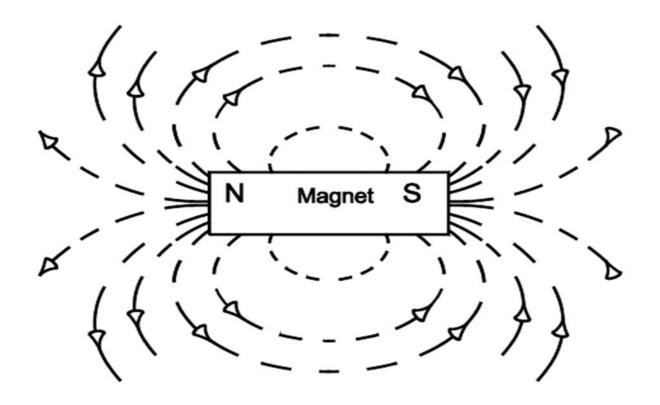

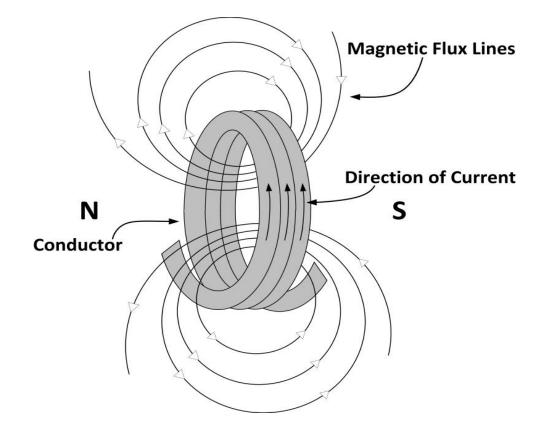
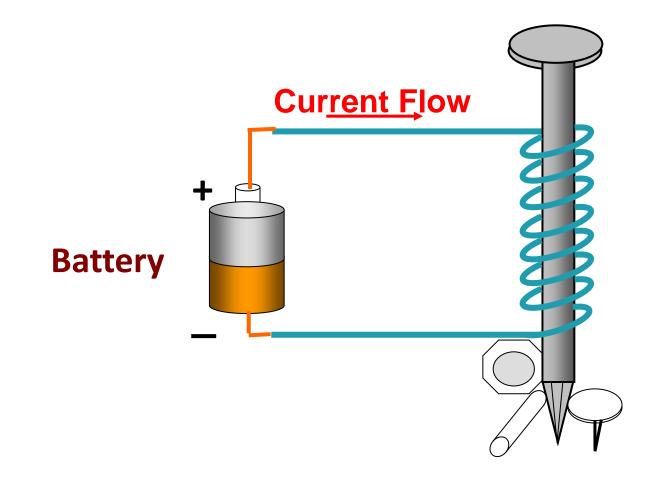
# Electric Theory, Quantities and Circuit Elements Electromagnet



W N C т RIC 0 0 R D I N ΑΤ G C 0 U N C \_\_\_\_


# Electric Theory, Quantities and Circuit Elements Electromagnetic Induction


In order to induce current and voltage you need 3-things:

- 1. Conductor
- 2. Magnetic field
- 3. Relative motion between the conductor and the magnetic field.
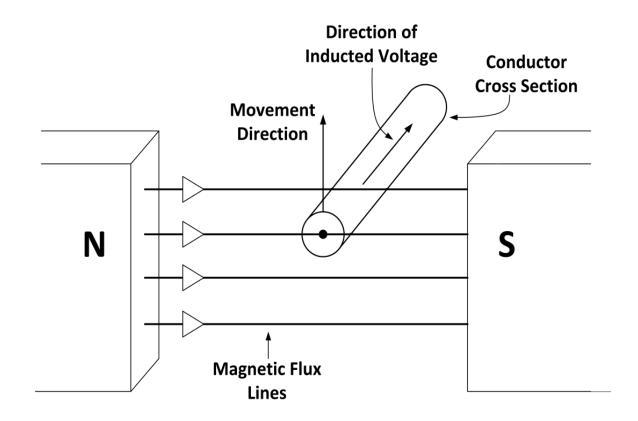
# **Creation of Voltage**

F С ΑΤ COUNC W N F С TRIC ТҮ OORDIN N G F S R - I. - I - I




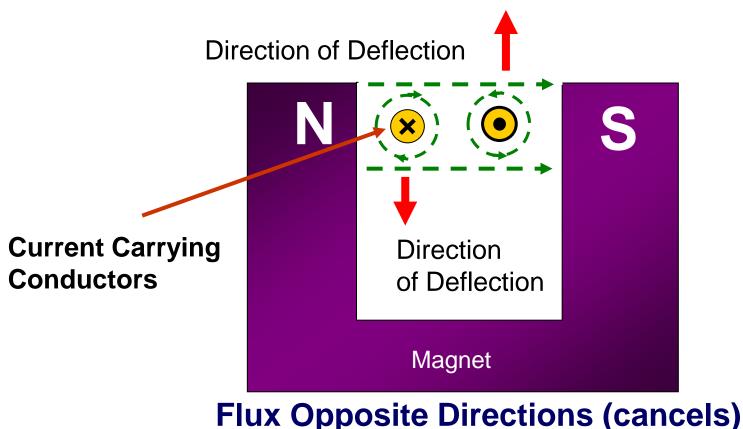

Flux the Same Direction (adds)

- Electromagnetic Induction creates a voltage or current in a conductor when a magnetic field changes
- In a *transformer*, alternating current in one winding *induces* a changing magnetic field in the transformer *core*
- The changing magnetic field *induces* an alternating voltage and current in the second winding

#### **Basic Transformer Operation**

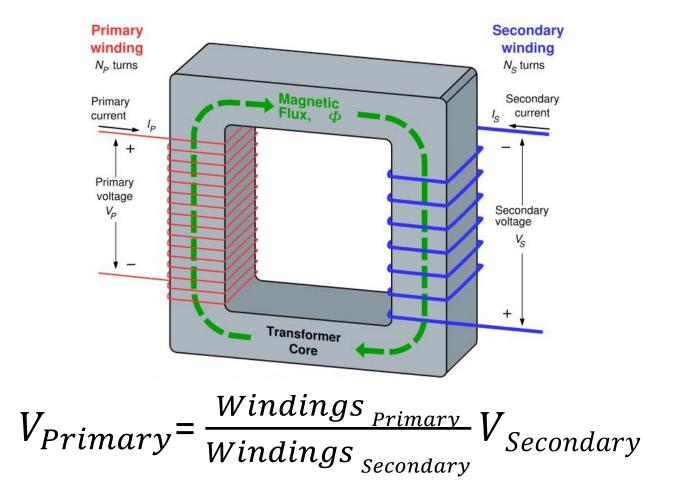


*Generator* - magnetic field of the rotor *Induces* a voltage in the stator windings.

- Rotor may be a permanent magnet
- In a large generator, the *rotor* is a spinning electromagnet – created by current from the exciter
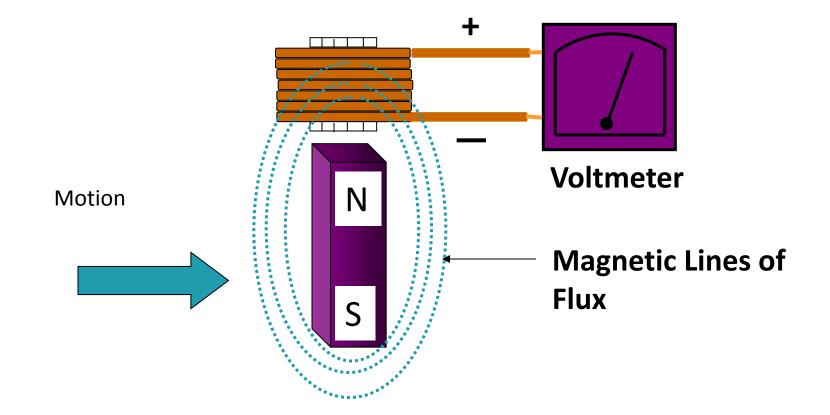
# Electric Theory, Quantities and Circuit Elements Electromagnetic Induction

Whenever a magnetic field is moved past a conductor a voltage is induced in the conductor



# Circuit Components and Properties



**Resistance (R)** is the property of materials that opposes or resists current by converting electric energy to heat.

- Unit of Measurement: ohms (Ω)
- A *Resistor* provides resistance to the circuit



Georg Ohm, 1789 -1854

#### **Resistance depends on:**

#### Resistivity

Conducting material has very low resistivity, insulators have very high resistivity.

#### Length

Decreasing the material's length decreases the resistance.

#### **Cross-sectional area**

Increasing the material's cross-sectional area decreases the resistance.

#### Temperature

The hotter the wire, the more resistance it exhibits.

Inductance (L) is the property of an electrical circuit that opposes change in current. The unit of inductance is the Henry (H).

- Any component that we use for its inductive property is called an inductor
- In the Power system, an inductor is sometimes also called a reactor

- An Inductor (L) is a coil of wire that creates a magnetic field when current is applied
- The changing magnetic field of an Inductor opposes the voltage that is trying to force current in the wire
- An inductor opposes a change in current

$$V = L \frac{dI}{dt}$$

(Voltage equals Inductor size times rate-of-change of Current)

**Capacitance (C)** is the property of an electrical circuit that opposes change in voltage.

Unit of Measurement: Farads(F)


A Capacitor stores electrical charge.

• A Capacitor consists of two metal plates separated by an insulating layer.

$$V = 1/(2\pi fC) \int Idt$$

(Voltage builds up as current flows into the Capacitor)


- The value of capacitance in a circuit is measured in capacitive units called farads.
- The farad is named after Michael Faraday, a 19th century British physicist, who is credited with developing the method of measuring capacitance.
- Farad determined that a capacitor has a value of one farad of capacitance if one volt of potential difference applied across its plates moved one coulomb of electrons from one plate to the other.

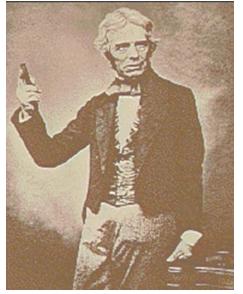

Michael Faraday

- A Capacitor consists of two conducting metal plates with an insulating sheet of material in between.
- When current is applied across the terminals, charge flows from one side to the other.
- Over time as **charge builds** on the capacitor, voltage increases.

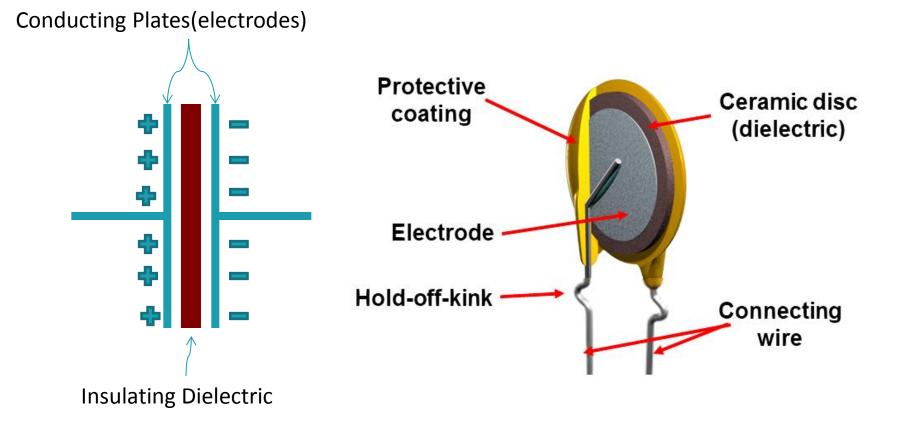
#### Electric Theory, Quantities and Circuit Elements Circuit Components and Properties: Capacitor Construction


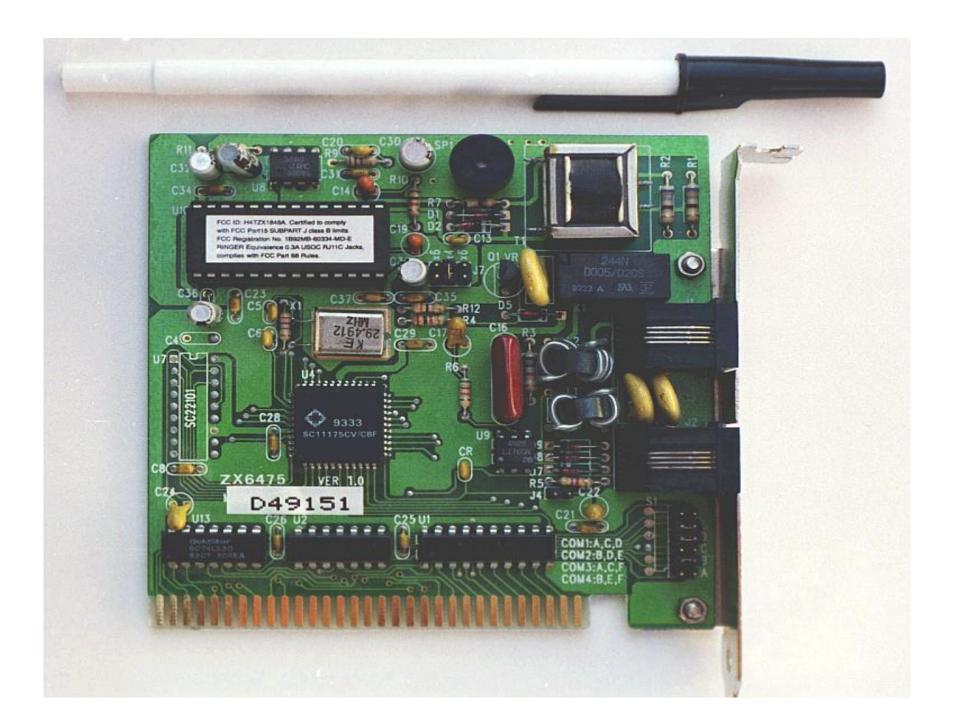
#### **Capacitors come in all sizes and shapes...**







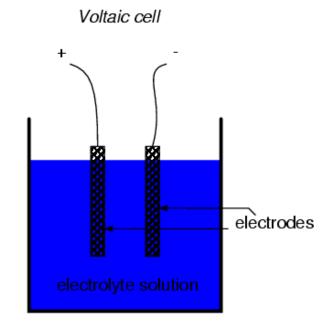
#### **Chemical Battery Operation**

In the battery, two different metals, called *ELECTRODES* are placed in a chemical solution called the *ELECTROLYTE*.

- The metals react differently.
- One loses electrons and develops a positive charge, the other attracts electrons and develops a negative charge.




#### Electric Theory, Quantities and Circuit Elements Circuit Components and Properties
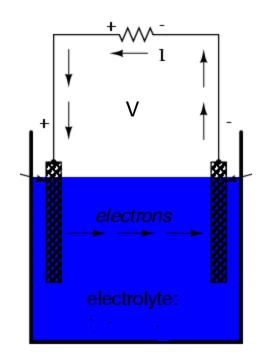
#### **Chemical Battery Operation**


This results in a DIFFERENCE IN POTENTIAL (Voltage) between the two electrodes.


When a conductor is attached to the electrodes of the battery, electrons flow from the *negative* electrode to the *positive* electrode.




#### Electric Theory, Quantities and Circuit Elements Circuit Components and Properties

#### **Chemical Battery Operation**

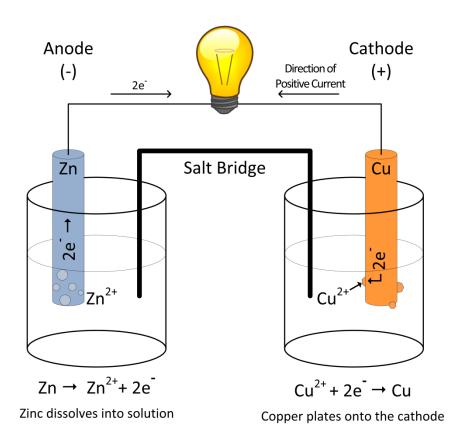


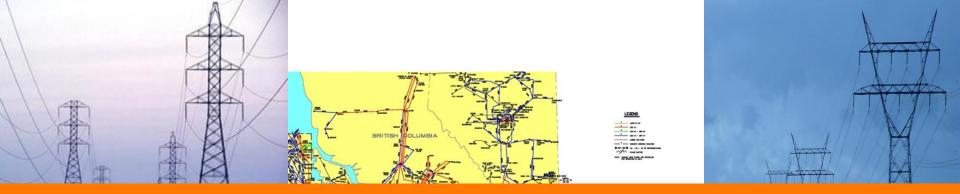


# **Circuit Analysis**

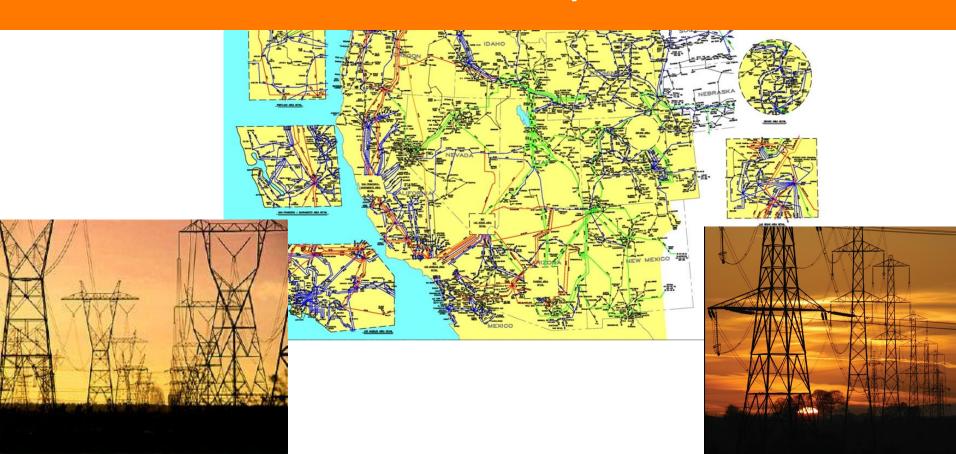
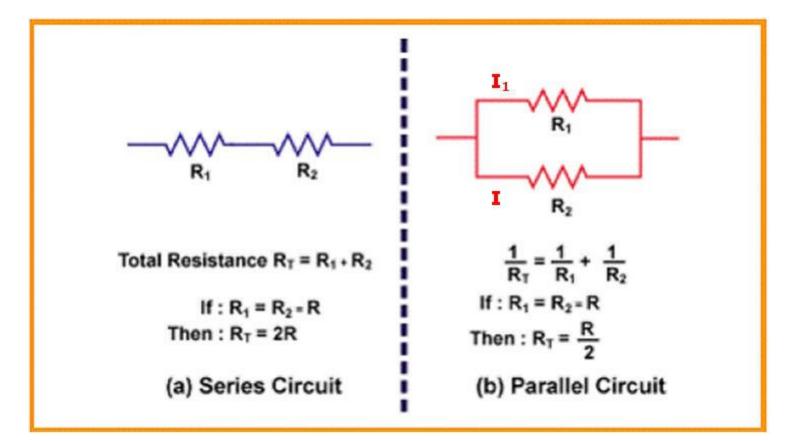
#### Electric Theory, Quantities and Circuit Elements Circuit Analysis - Series and Parallel Circuits



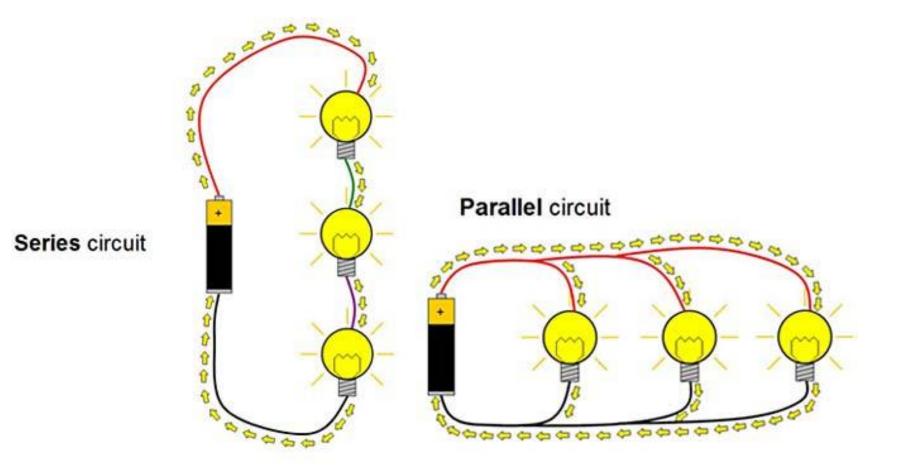
### Electric Theory, Quantities and Circuit Elements Circuit Analysis: Series and Parallel Circuits



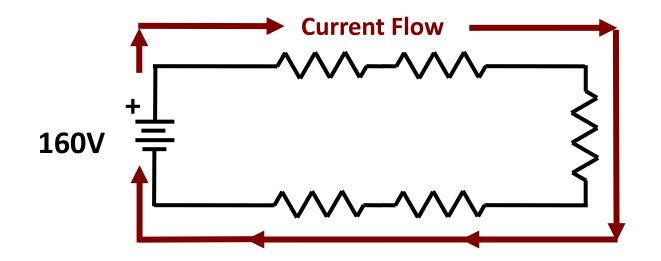
# Electric Theory, Quantities and Circuit Elements Circuit Analysis: Series Circuit

A series circuit is a circuit that has only one path for current to flow.



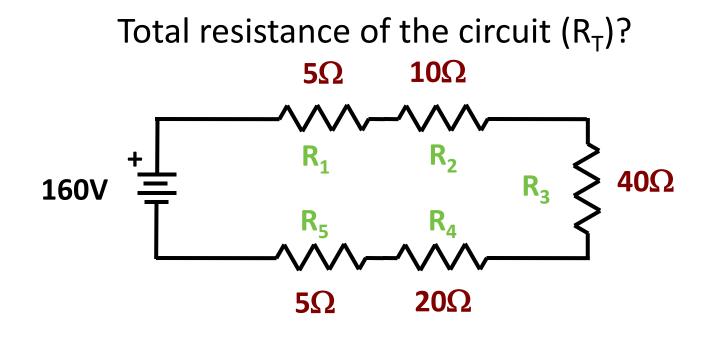
### Electric Theory, Quantities and Circuit Elements Circuit Analysis: Series Circuit




 $R_{T} = R_{1} + R_{2} + R_{3} + R_{4} + R_{5}$   $R_{T} = 5 \Omega + 10 \Omega + 40 \Omega + 20 \Omega + 5 \Omega$   $R_{T} = 80 \Omega$ 
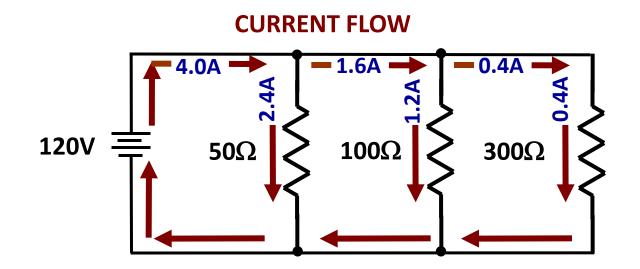
# Electric Theory, Quantities and Circuit Elements Circuit Analysis: Parallel Circuit

A parallel circuit is a circuit that has more than one path for current to flow.


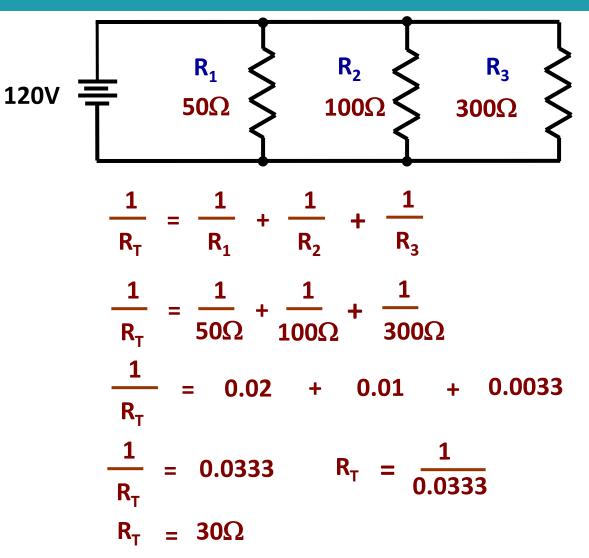
### Electric Theory, Quantities and Circuit Elements Circuit Analysis: Parallel Circuit



Ohm's Law and Kirchoff's Law

# Electric Theory, Quantities and Circuit Elements Ohm's Law

#### Ohm's Law:

– Voltage Drop = Current \* Resistance

# **Kirchhoff's Laws:**

- Sum of current entering a junction equals the sum of current leaving the junction.
- Sum of voltage drops equals the applied voltage.

### Electric Theory, Quantities and Circuit Elements Ohm's Law



Ohm's law, named after Mr. Georg Ohm, a German mathematician and physicist. 1789 -1854.

He defined the basic relationship between power, voltage, current and resistance.

The principles apply to AC, DC or RF (radio frequency).

# Electric Theory, Quantities and Circuit Elements Ohm's Law


V = IR I = V/R R = V/I

#### Where:

- V = Voltage *in Volts*
- I = Current *in Amps*
- **R** = Resistance *in Ohms*


WESTERN ELECTRICITY COORDINATING COUNCIL
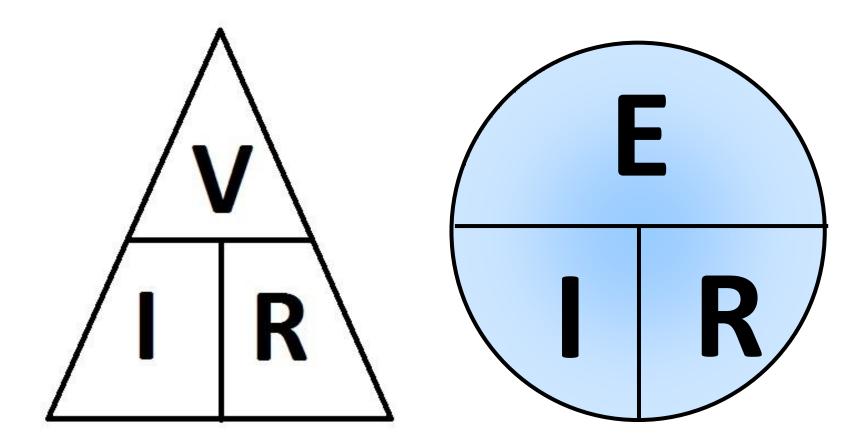
# Electric Theory, Quantities and Circuit Elements Ohm's Law: Pie or Triangle



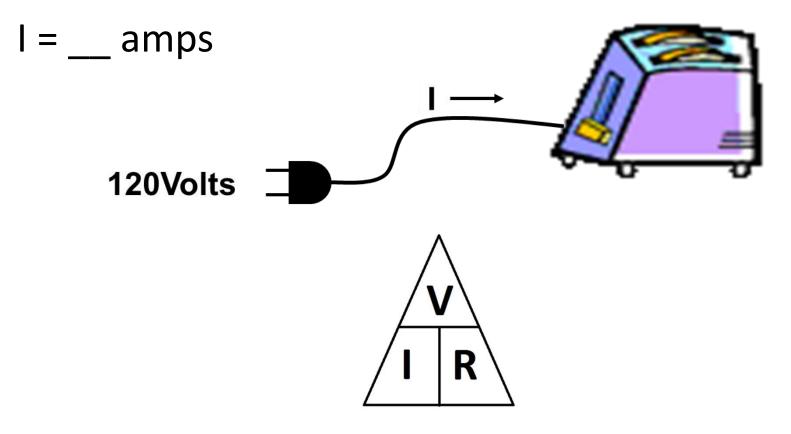
# Electric Theory, Quantities and Circuit Elements Quick question

How much current is flowing in the toaster circuit?


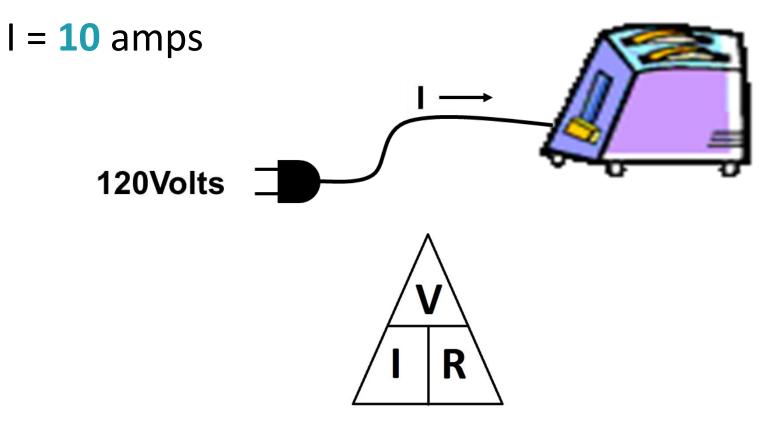
# Electric Theory, Quantities and Circuit Elements Quick question

How much current is flowing in the toaster circuit?




# Electric Theory, Quantities and Circuit Elements Kirchoff's Law

**Kirchhoff's Current Law:** the sum of the currents entering a junction equals the sum of the currents leaving a junction.

- For series circuits the current is the same at all points
- For parallel circuits the total current in a parallel circuit is equal to the sum of the currents in each branch
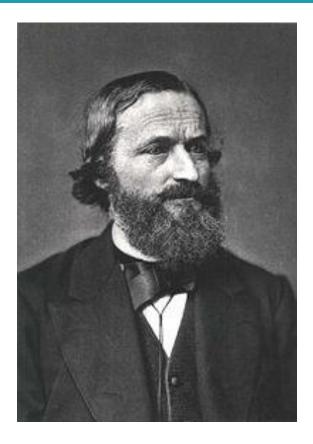
## Electric Theory, Quantities and Circuit Elements Kirchoff's Law



Gustav Kirchoff was a German Physicist 1824 – 1887.

He developed laws for circuit analysis as well as other laws for "black body" radiation and thermochemistry.

# Electric Theory, Quantities and Circuit Elements Kirchoff's Law

Kirchhoff's Voltage Law states:

- The voltage difference across a resistor is called a voltage drop
- In series circuits, the sum of the voltage drops around the circuit is equal to the applied voltage
- In parallel circuits, the voltage drops across all the branches are the same

# Check Your Knowledge: Fundamentals of Electricity

- 1. A blow drier uses 120 Volts and draws 10 amps. What is its resistance?
- 2. How much power does it use?
- 3. How much would it cost to run the blow drier for one hour?
- 4. If you had two similar blow dryers plugged in to the wall would they be in series or parallel?
- 5. How many amps total would they use?
- 6. If you re-wired the blow dryers to put one in series with the other, what would be the total resistance?
- 7. How much current would flow through the circuit?
- 8. What would the voltage across each dryer be?
- 9. What would be the total power used?

#### **Alternating Current**

- Generating AC Current
- Sine Waves
- RMS Values
- Phase Relationship
- Right Triangle Relationships
- Impedance–Resistance, Inductance, Capacitance


### Alternating Current (AC)


Alternating Current (AC) periodically changes direction of flow and magnitude.


- AC voltage produces an alternating current
- AC power is produced by alternating current and alternating voltage


# **Generating AC Current**


WESTERN ELECTRICITY COORDINATING COUNCIL

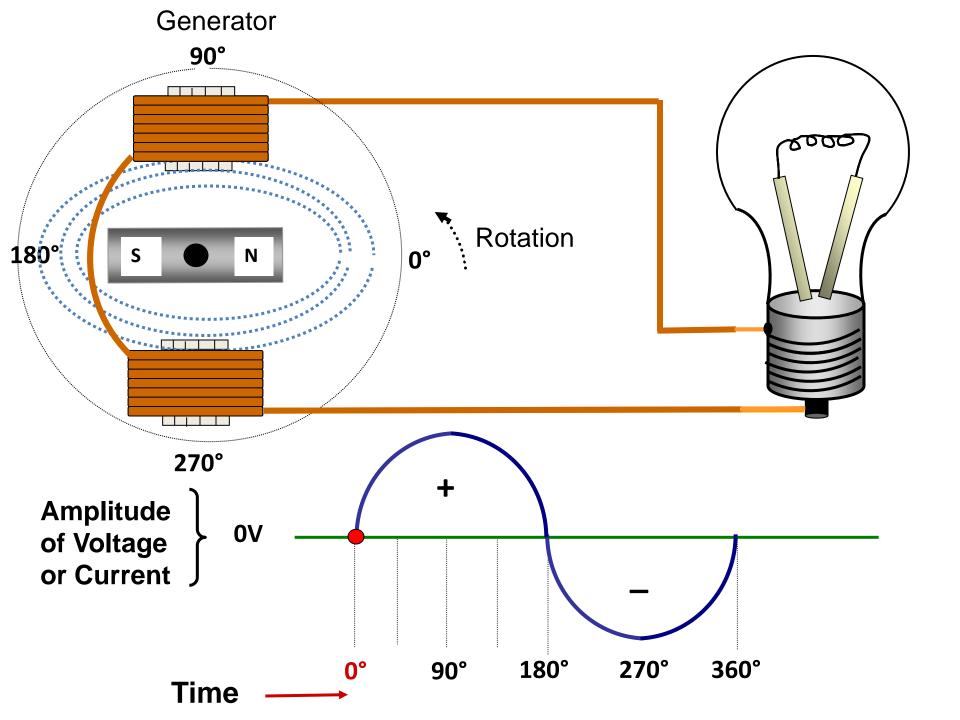


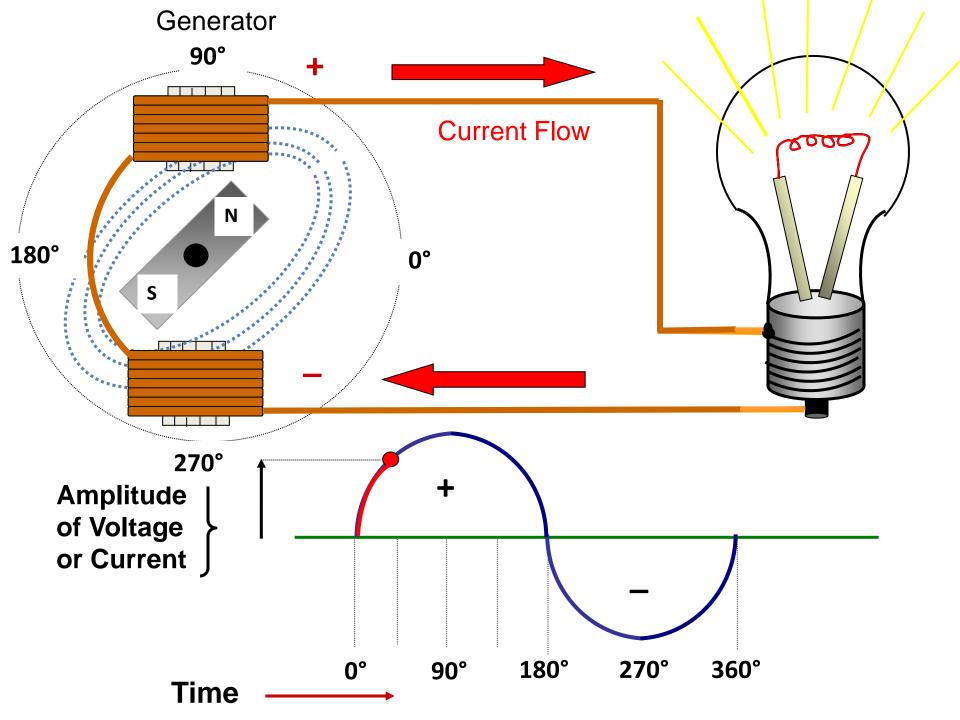


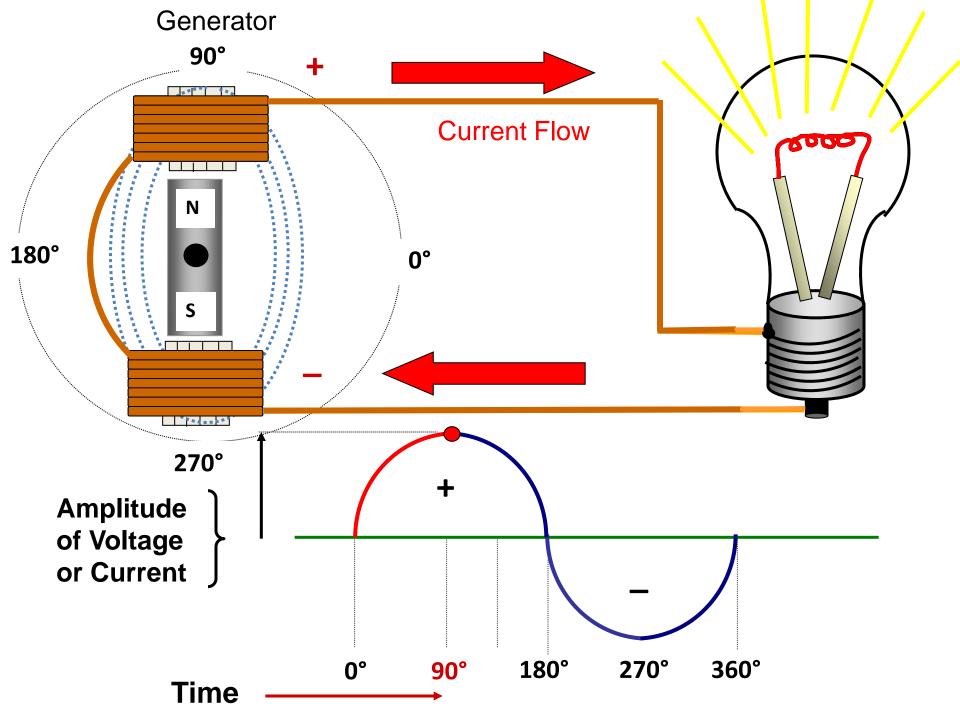


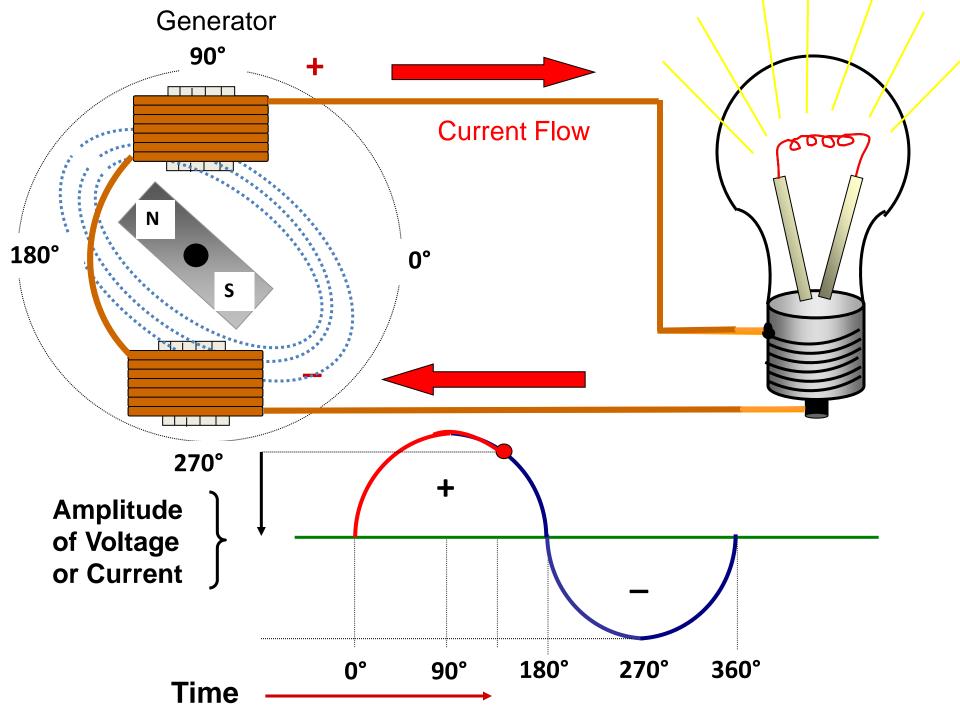


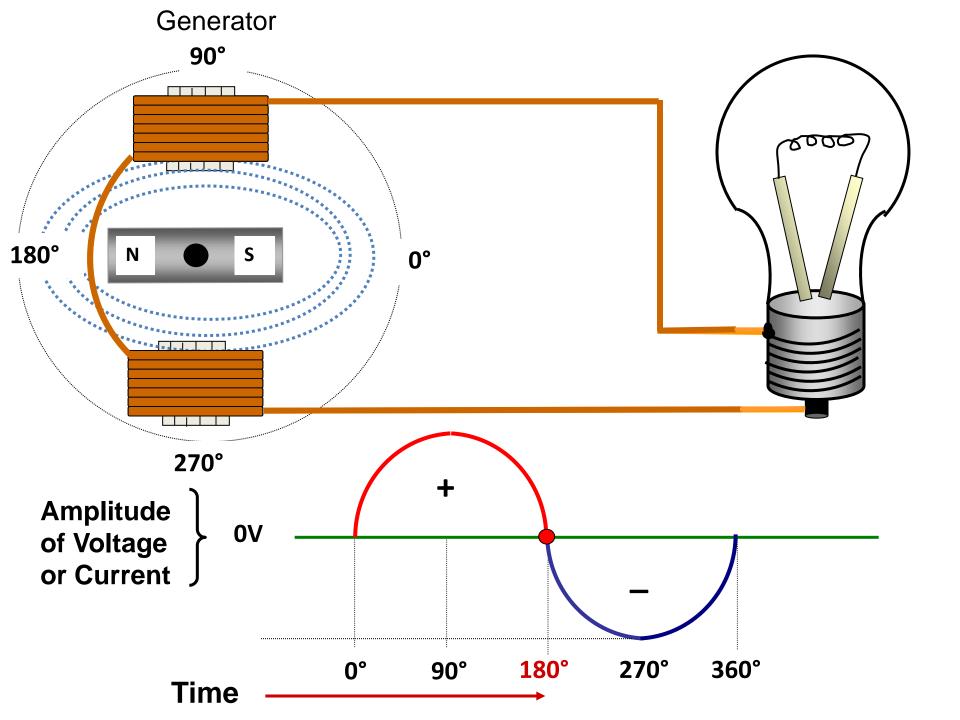

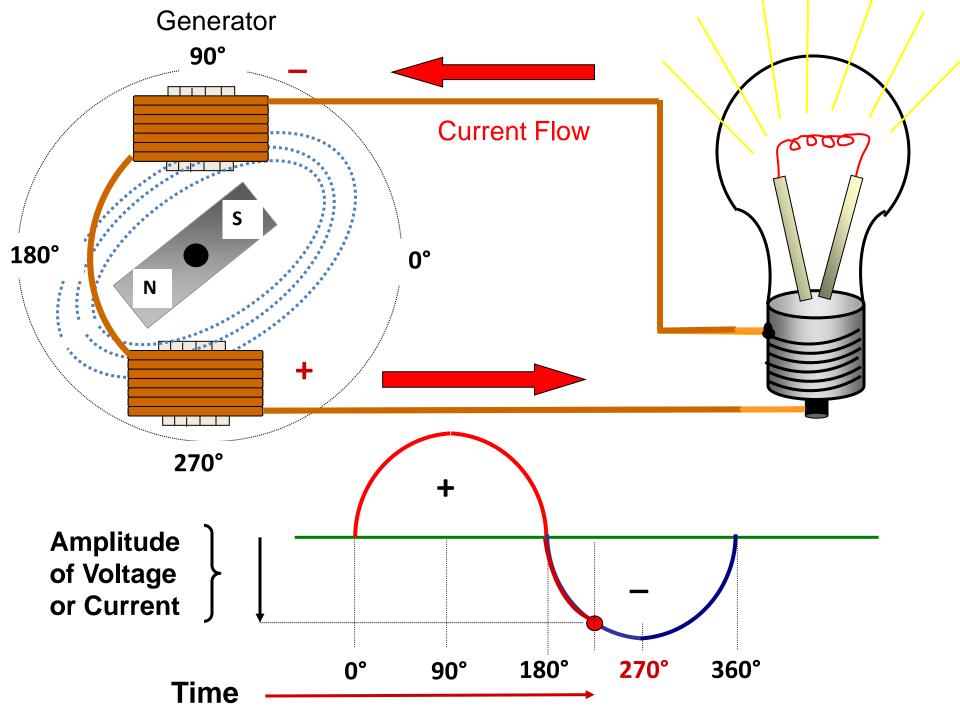

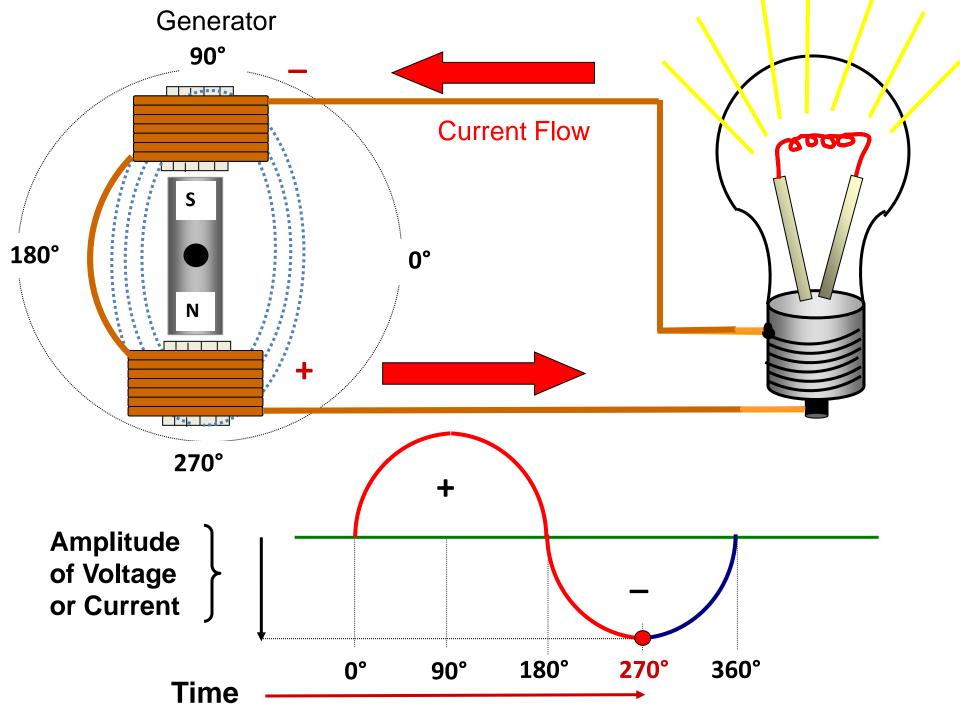

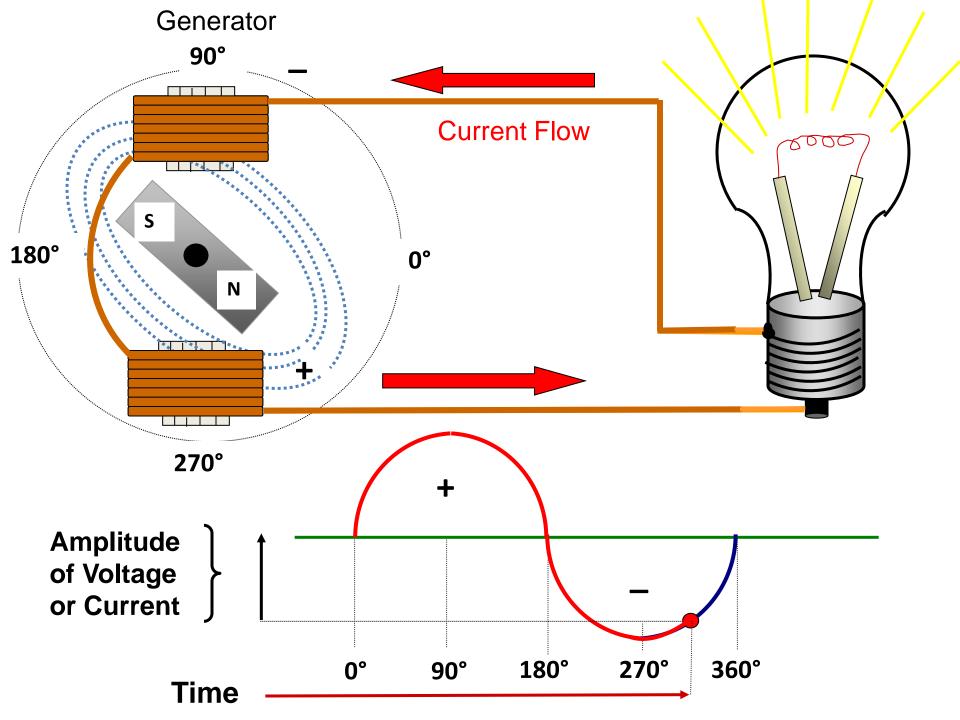

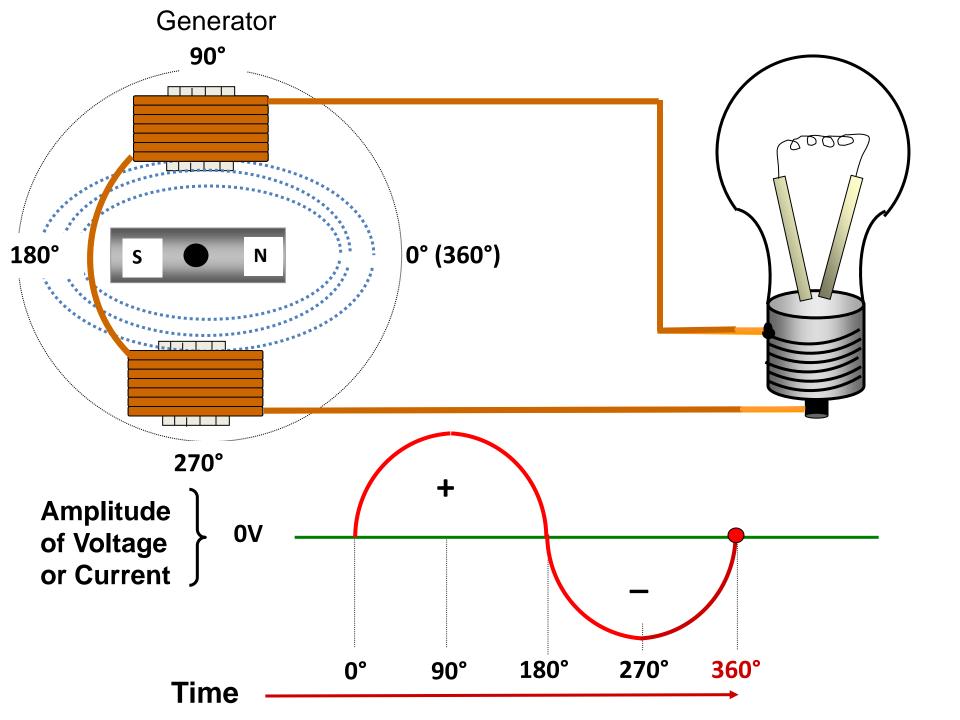


# Sine Waves

WESTERN ELECTRICITY COORDINATING COUNCIL


Alternating Current (AC) Sine Waves

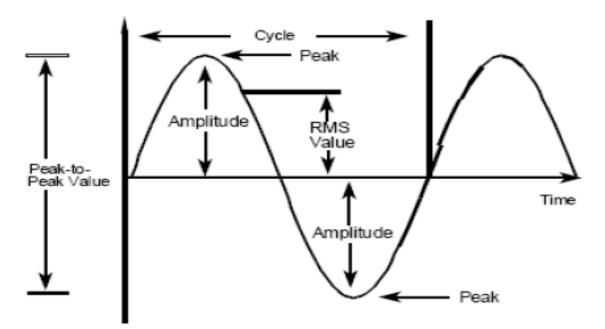A Sine Wave is a curve that describes a smooth repetitive oscillation.




Alternating Current (AC) Sine Waves

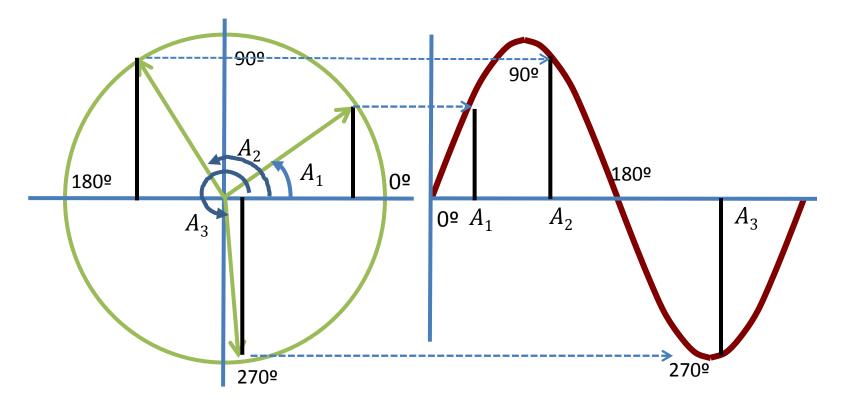A Sine Wave shows the height of the circle at a given angle.


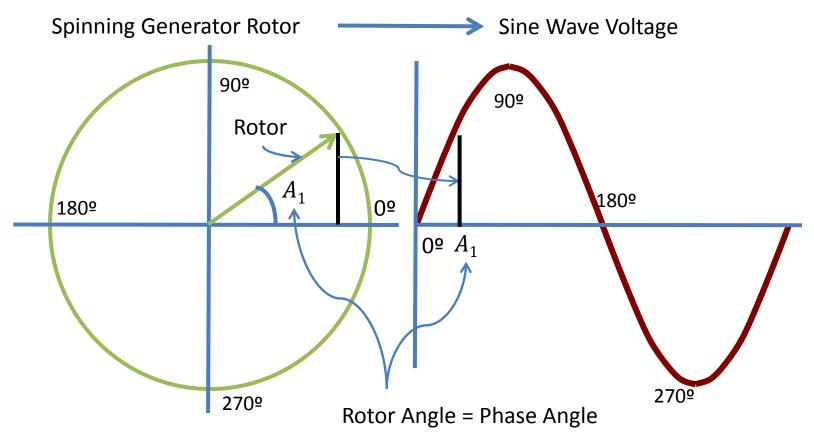
### Alternating Current (AC) Sine Waves

Spinning Generator Rotor creates a Sine Wave Voltage



A Cycle is the part of a waveform that does not repeat or duplicate itself. In the time it takes to complete one cycle, the current:

- ✓ builds from zero to the maximum amplitude in one direction
- ✓ decays back to zero
- ✓ builds to the maximum amplitude in the opposite direction
- ✓ decays back to zero again

- The Period (T) is the time required to complete one cycle
- Frequency (f) is the rate at which the cycles are produced
- Frequency is measured in Hertz (Hz). One hertz equals one cycle per second


Frequency (f) and period (T) are related by the following equations:

$$f = 1/T$$
$$T = 1/f$$

#### Amplitude

- peak
- peak-to-peak
- RMS (Effective Value)
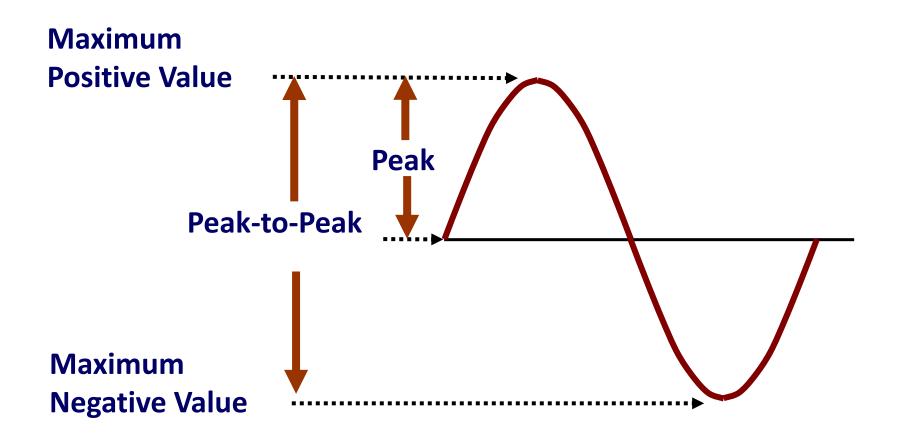
#### Alternating Current (AC) AC Power Sine Wave



# **RMS Values**

## Alternating Current (AC) RMS (Effective) Value


- The effective or root mean square (RMS) is the amount of AC current or voltage that has the same effect as a given amount of DC current or voltage in producing heat in a resistive circuit
- Effective value (RMS) is the most common way of specifying the amount of AC
- One amp of effective AC and one amp of DC produce the same power when flowing through equal resistors

Alternating Current (AC) RMS Values


- The Root Mean Square (RMS) Value is the Effective value
- To calculate the RMS value of a waveform,
   Square the instantaneous values over one period, average them to provide the Mean, and take the square Root of the mean
- RMS value is 70.7% of Peak value

$$I_{rms} = \frac{\sqrt{2}}{2} I_p = .707 I_p$$

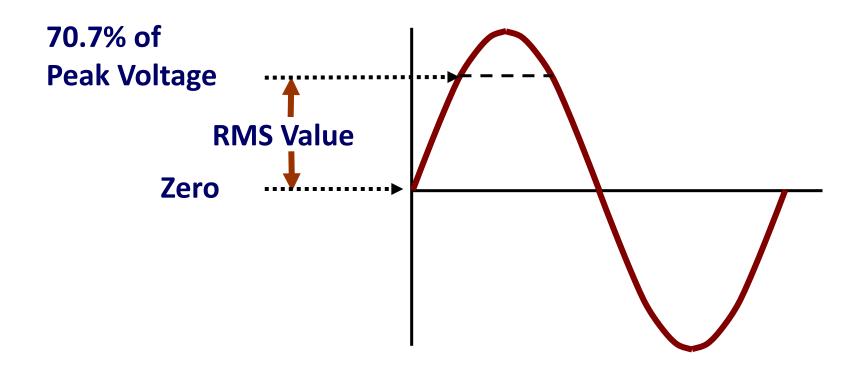
#### Alternating Current RMS (Effective) Value


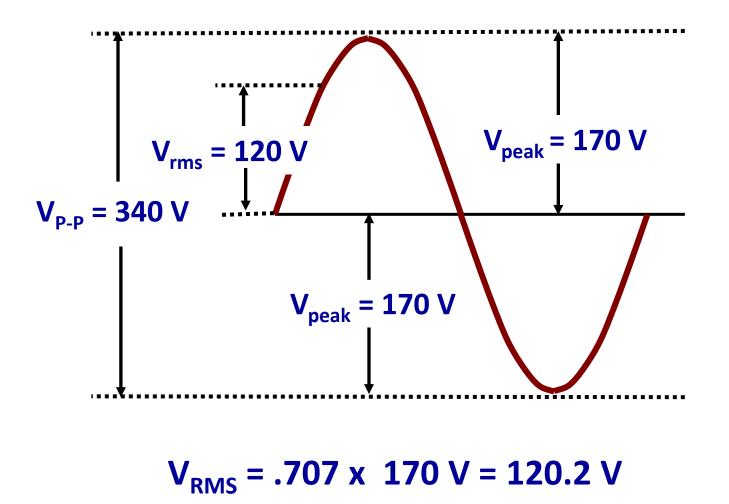
#### Alternating Current Household Voltage


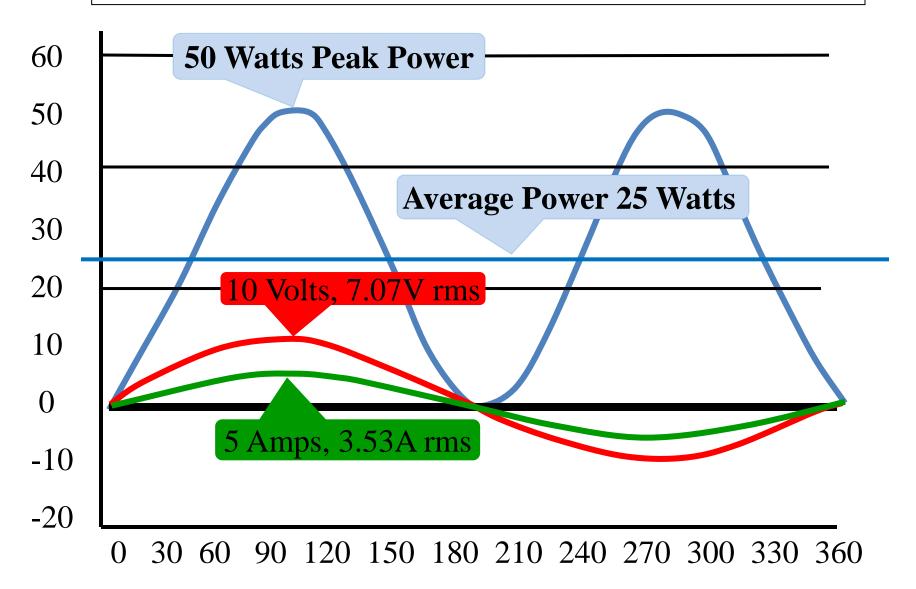
#### **RMS Voltage \* RMS Current = Average Power**




# Phase Relationship

Phase Angle is the angle difference between two sine waves with the same frequency


- Phase Angle is sometimes called *phase relation*
- *Phase angle* is the portion of a cycle that has elapsed since another wave passed through a given value

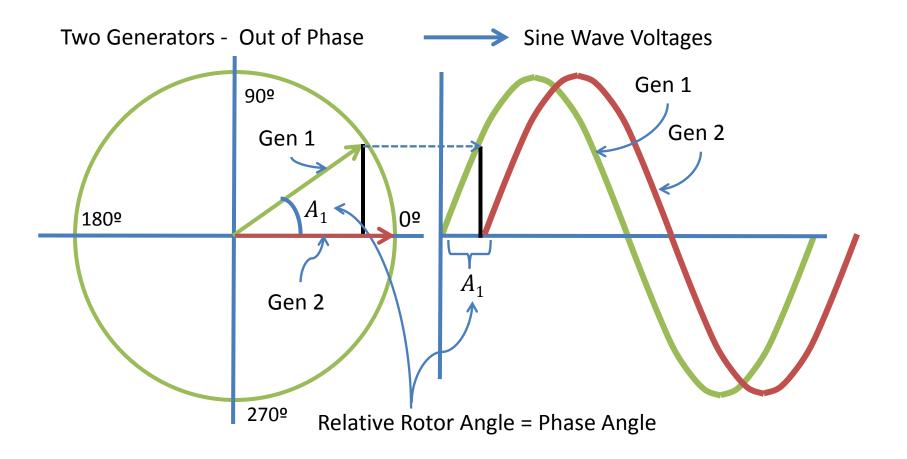
#### Alternating Current (AC) Phase Angle Between Two Generators


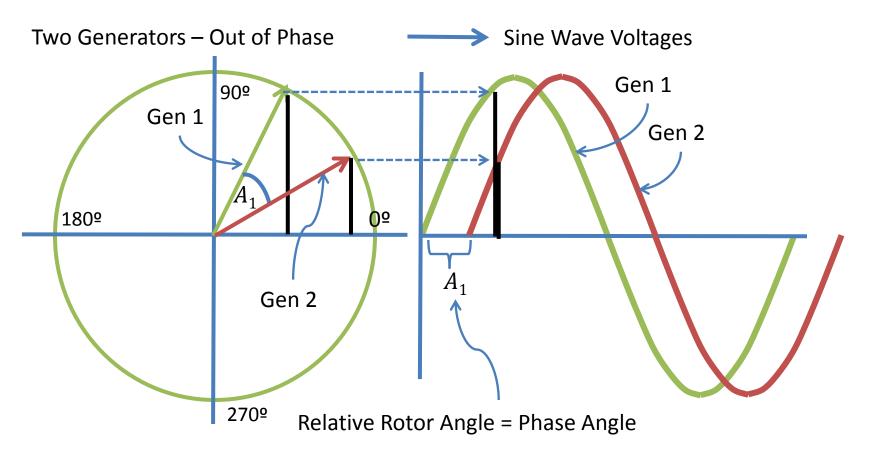
#### Alternating Current (AC) Phase Angle Between Two Generators

Angle between Generators stays the same while they both rotate



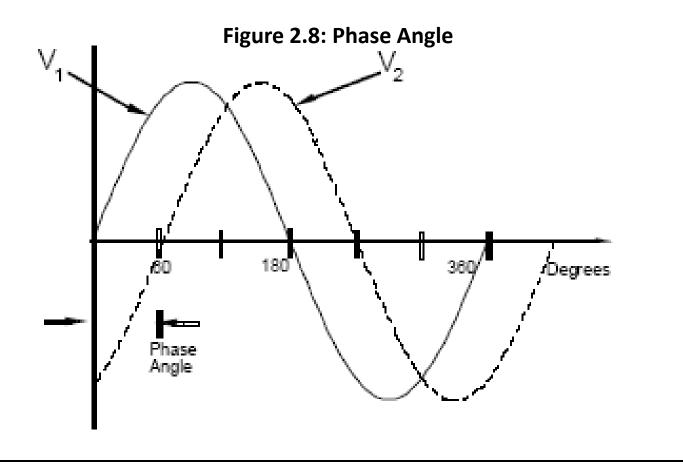

 $V_1$  = Generator #1  $V_2$  = Generator #2

## Alternating Current (AC) Phase Angle Between Two Generators

In-Phase - the phase angle between two generators is zero degrees

The generated voltages cross zero at the same time

## Alternating Current (AC) Phase Angle Between Two Generators

**Out-of-Phase** means that the phase angle between two generators is not zero degrees.

- The generated voltages cross zero at different times
- Only applies if the two waveforms have the same frequency


A **phasor** is a line representing a rotating quantity (voltage or current) for which:


- ✓ Length represents magnitude
- ✓ Direction represents the phase angle (in electrical degrees)
- ✓ Zero electrical degrees are on the right side of the horizontal axis
- ✓ Rotation is counterclockwise

A **phasor** is similar to an arrow drawn on the end of a spinning shaft

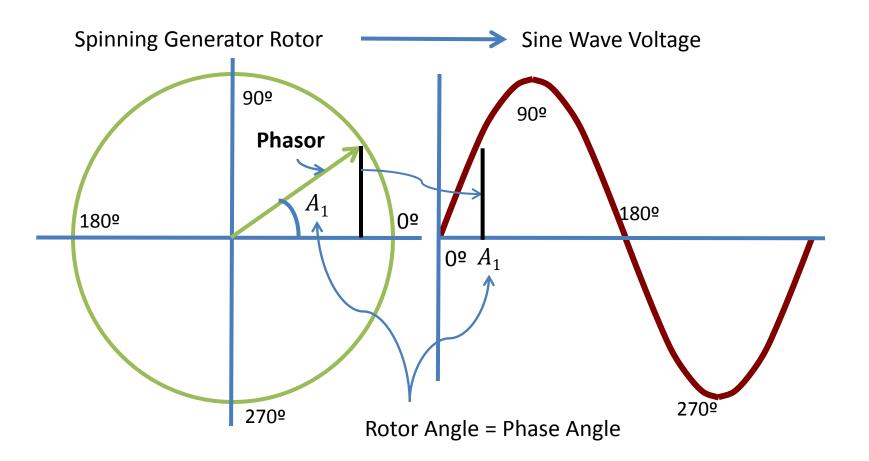• A strobe light flashes once each time the shaft does a full revolution






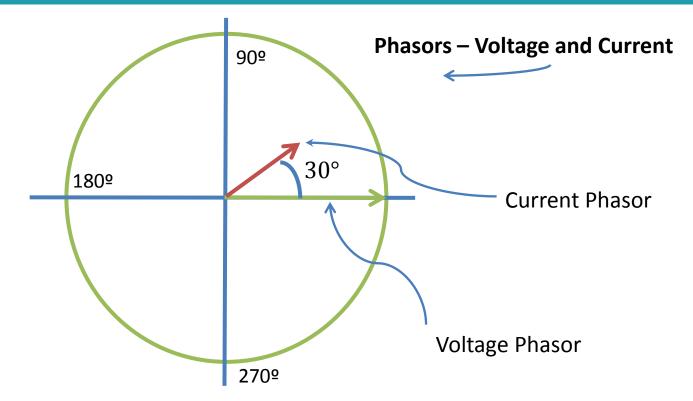

Since phasors rotate in a counterclockwise direction, the phasor diagram above shows the current leading the voltage by 30<sup>o</sup>.

# **Right Triangle Relationships**

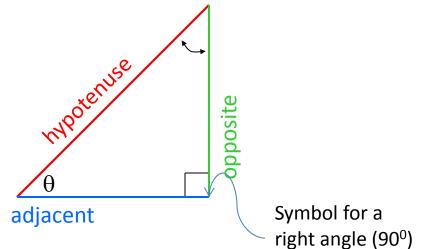
# A Right Triangle has one corner with a 90<sup>o</sup> Angle.




The right triangle can be used to represent:


- Resistance vs Reactance
- Real versus Reactive portion of Current and Voltage
- Real and Reactive Power

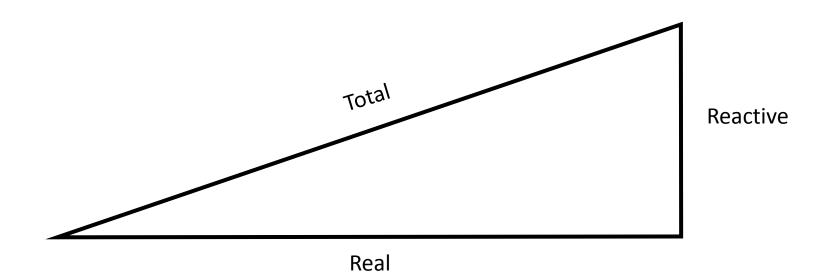The right triangle can be used to represent the resistive, reactive, and Resulting total.




#### Angles total 180<sup>o</sup>

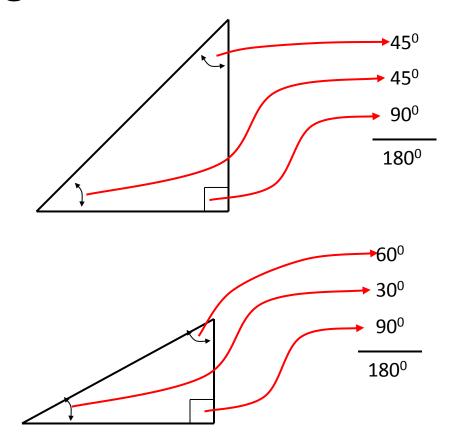


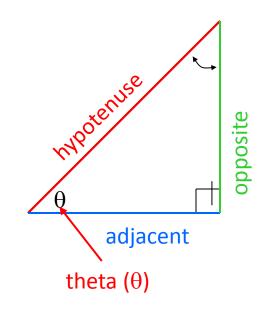


# **Right Triangles**

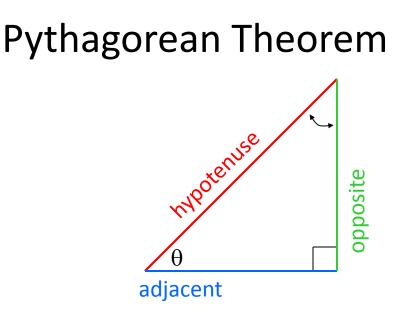

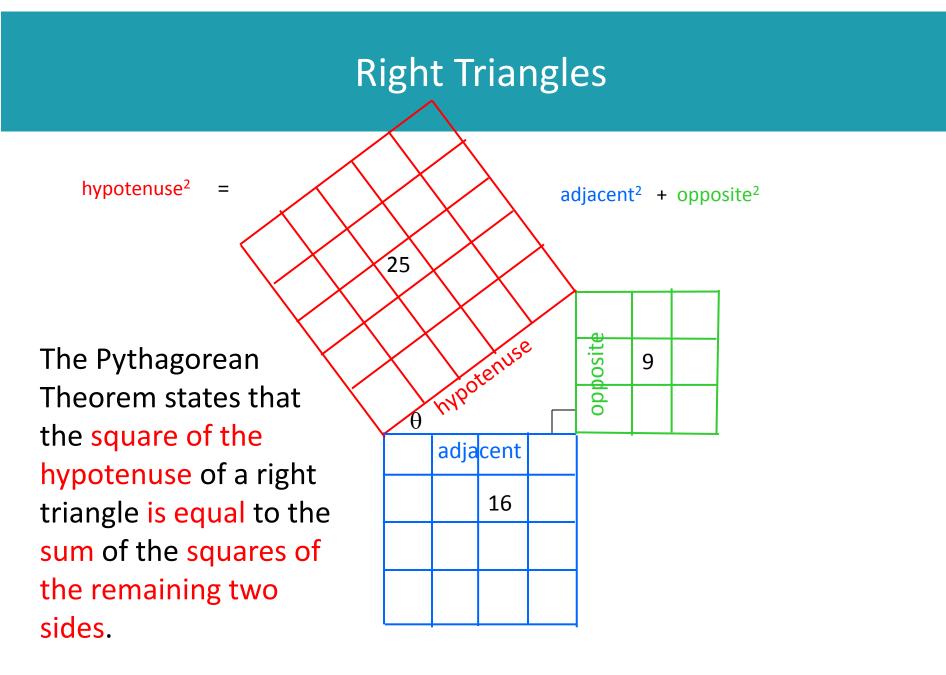
The Pythagorean Theorem states that the square of the hypotenuse of a right triangle is equal to the sum of the squares of the remaining two sides.



#### Pythagorean Theorem

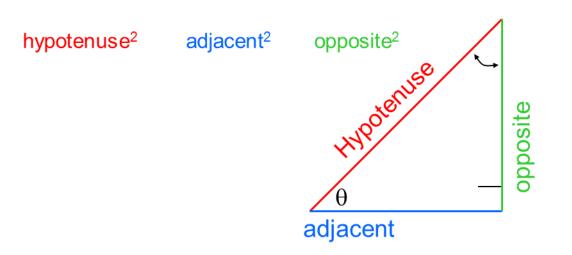


#### Pythagorean Theorem

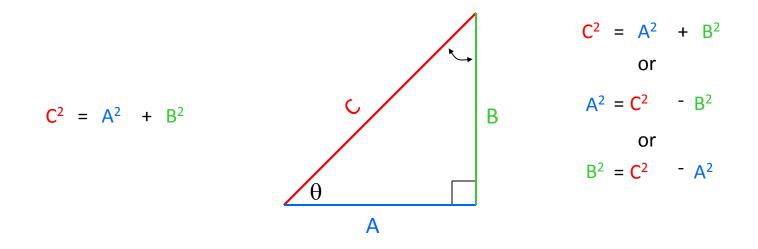


Using our formula, we could find the value of any side if we know the value of the other two sides.

Pythagorean Theorem

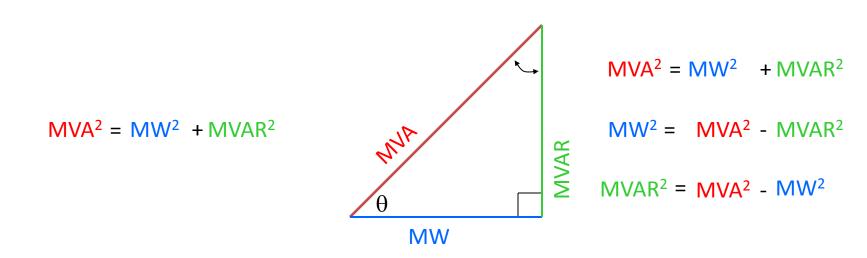


Generators produce Mega-Watts and Mega-Vars. Use the right triangle to find the values.

#### Pythagorean Theorem

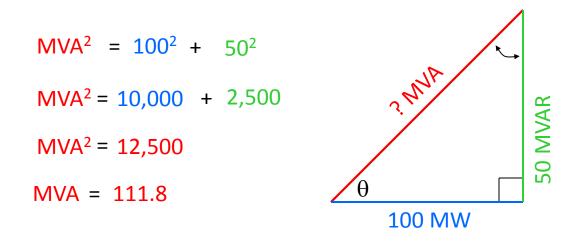


If a generator was producing 100 MW and 50 MVAR we could calculate the MVA using our formula.

#### Sine and Cosine

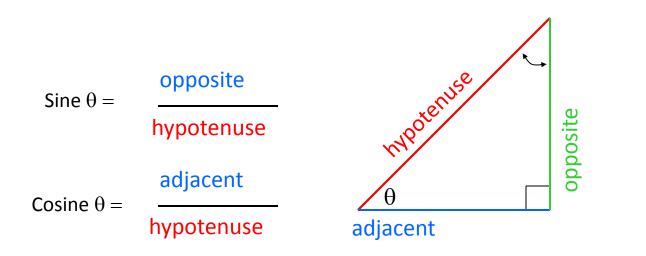


#### Sine and Cosine

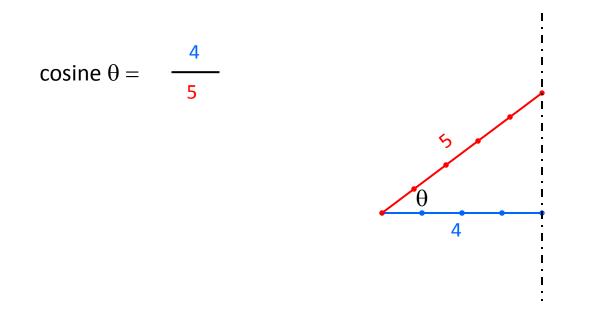


This ratio of Adjacent side to Hypotenuse establishes the slope of the angle


#### Sine and Cosine

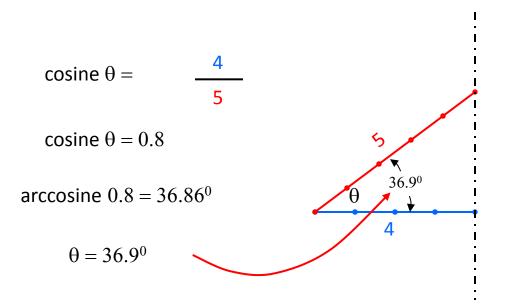


Determine the angle theta using the inverse of the cosine of theta the arccosine.


#### Sine and Cosine

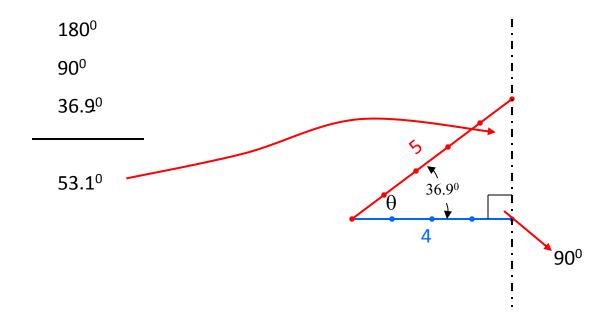

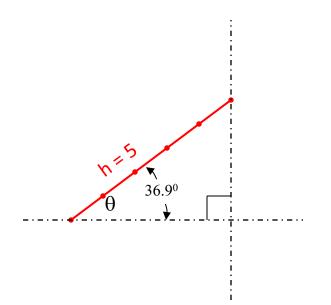

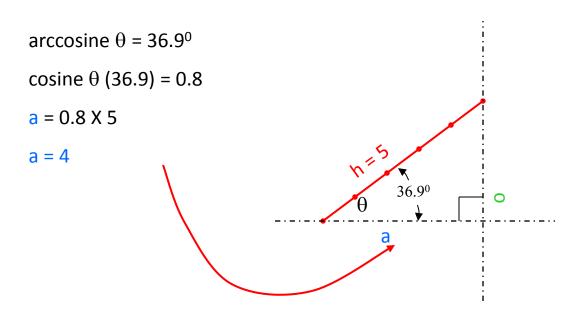
We can solve for all angles and sides given only one side and one angle



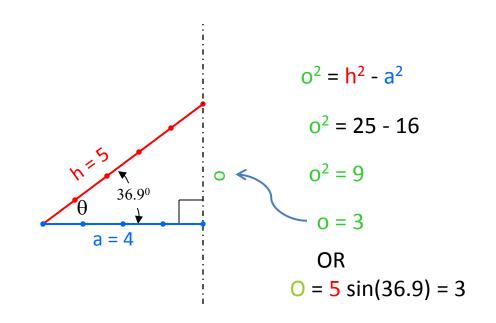

Summary


- A right triangle has one right angle (**90**<sup>°</sup>)
- The sum of the angles of any triangle equals **180**°
- The sides of a right triangle are named the hypotenuse, adjacent and opposite side.
- The hypotenuse of any right triangle will always be the longest side.
- The square of the hypotenuse is equal to the sum of the squares of the remaining two sides
- The **sine** equals the ratio of the opposite side to the hypotenuse
- The cosine equals the ratio of the adjacent side to the hypotenuse

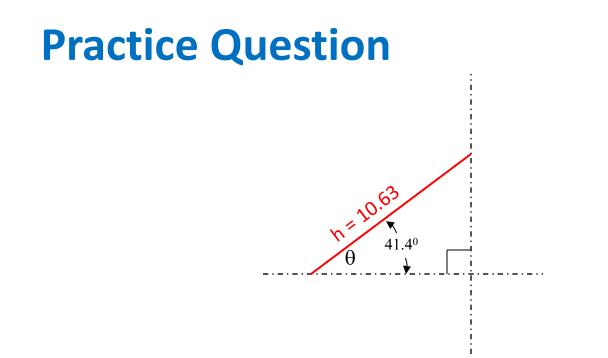

Solve the unknown sides and angles of this right triangle using the methods we have learned in this module on right triangles.

#### **Application to Electricity**

Resistive, Reactive, and Total Impedance

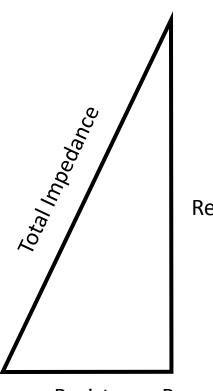


Reactance X

Resistance R

Application to Electricity

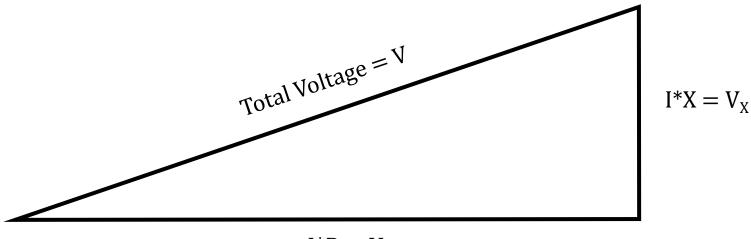
Total Voltage drop equals the voltage drop across resistor squared plus voltage drop across reactor squared.



 $I^*R = V_R$ 
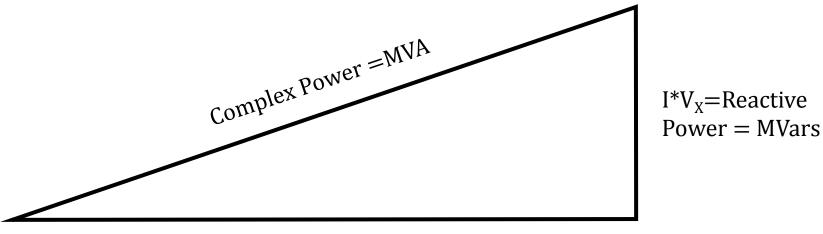
#### **Application to Electricity**

Apparent Power = Real Power + Reactive Power (Vars)



 $I*V_R$ =Real Power =MWatts

# Check Your Knowledge: Fundamentals of Electricity


- 1. In a right triangle with the adjacent side equal to 5 and the opposite side equal to 12, what is the length of the hypotenuse?
- 2. Can you prove graphically that the Pythagorean Theorem is true?
- 3. What is the sine of 45 degrees?
- 4. With a hypotenuse of one and an adjacent side of .5, what is the angle? The opposite side?

# Impedance Resistance, Inductance, Capacitance

157

Impedance (Z) is the total opposition to current.

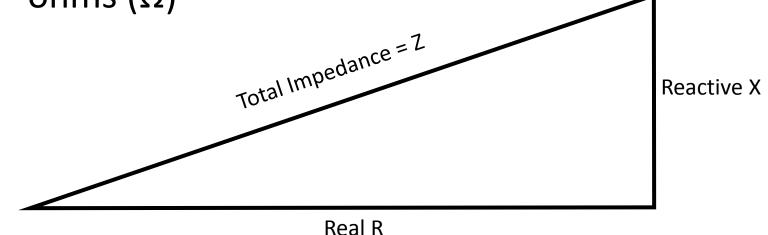- Impedance is the vector sum of the resistance and reactance
- Impedance is represented by a Z and measured in ohms ( $\Omega$ )



- Impedance of *resistors* is independent of whether the current is AC or DC
- Impedance of *inductors* and *capacitors* depends on the rate-of-change or frequency of the voltage


- Impedance of capacitors and inductors is also called reactance
- Reactance depends on frequency

$$X_C = rac{1}{2\pi f C}$$
 - Current Leads the Voltage  $X_L = 2\pi f L$  - Voltage Leads the Current

Inductive Reactance( $X_L$ ) opposes change in current. It is measured in ohms( $\Omega$ ).

- Reactance does not convert the electrical energy into heat energy
- The reactor **temporarily stores the energy** in the expanding magnetic field, then gives it back when the field collapses

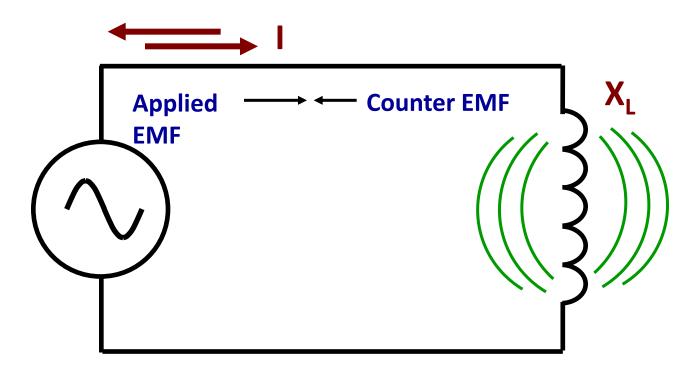Inductors are devices that oppose *changes* in current flow using a magnetic field.




This form of Ohm's Law applies to inductive reactance:

$$V = IX_L$$


Where:

- V and I = Voltage and current, respectively
- $X_L = 2\pi f L$ = Inductive Reactance
- $\pi$  = Constant (approximately 3.14)
- f = Frequency
- L = Inductance

The Current lags the voltage by 90°

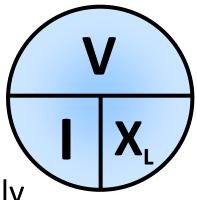


## Inductance

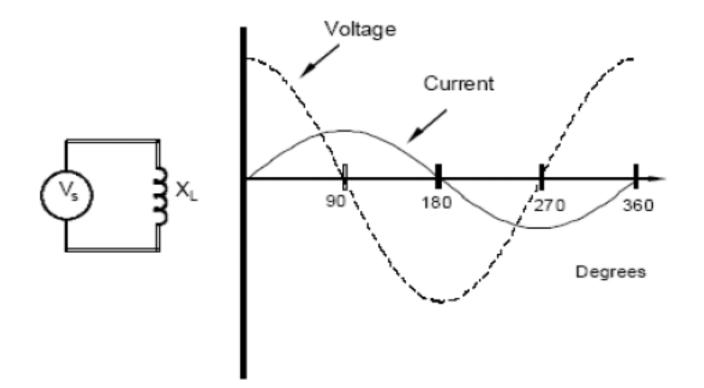

The current lags the voltage by 90° in this example.

Alternating Current (AC) Inductance
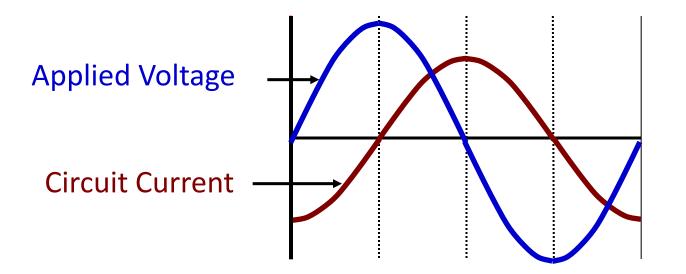
#### **Current Lags Voltage by a Maximum 90°**



The maximum amount that the inductance can cause the current to lag behind the voltage is 90°

#### ELI the ICE man


(A catchy memorable phrase)

#### Voltage leads the current in an inductive circuit.

#### ELI

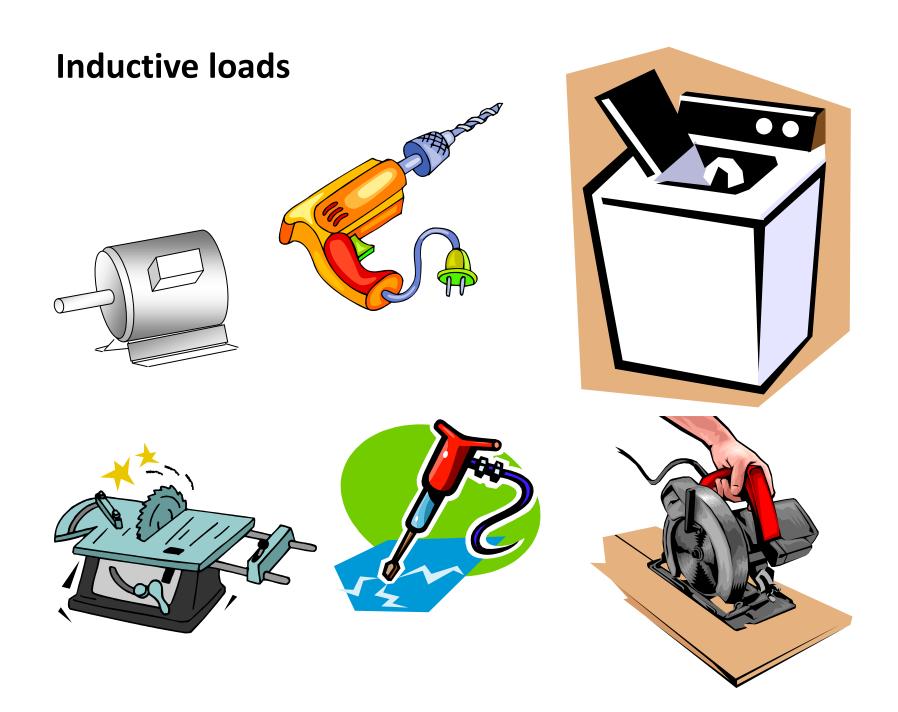
#### **E** = Voltage **L** = Inductance **I** = Current

(The hard part is remembering why I=Current and E=Voltage)







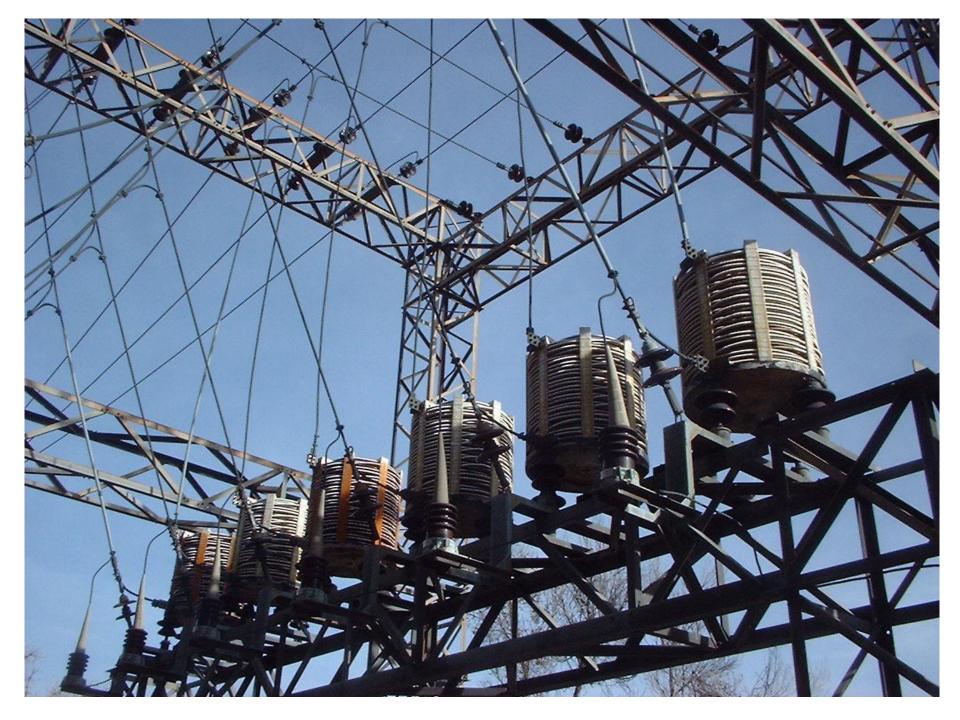






Capacitive Reactance  $(X_c)$  opposes change in voltage. It is measured in ohms $(\Omega)$ .


- Reactance does not convert the electrical energy into heat energy
- The capacitor **temporarily stores the energy** in the electric field between its plates, then gives it back when the field collapses

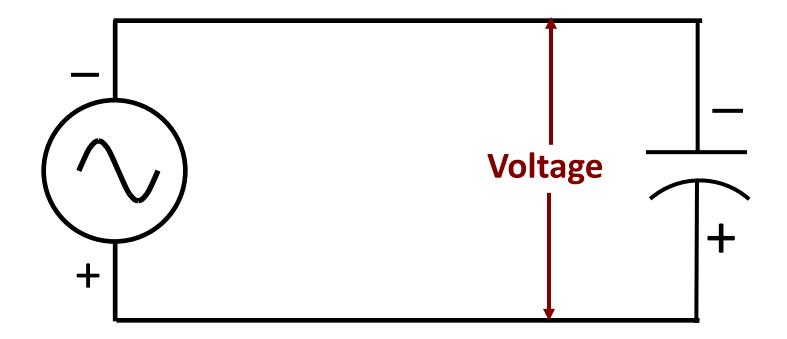Capacitors are devices that store electrical charge. They *oppose a change of voltage*.



The following form of Ohm's Law applies to capacitive reactance:

$$V = IX_C$$

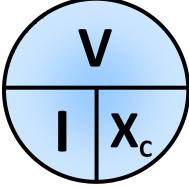

Where:

- V and I = Voltage and current, respectively.
- $X_C = 1/(2\pi f C)$ = Capacitive Reactance
- $\pi$  = Constant (approximately 3.14)
- f = Frequency
- C = Capacitance

Current can lead the voltage by up to 90<sup>o</sup>.

Similar to inductive reactance, capacitive reactance depends on frequency.

Increasing the frequency *decreases* the capacitive reactance.

#### **Definition:** Susceptance

- There are times when using the reciprocal of X<sub>C</sub> makes calculations easier
- The reciprocal of X<sub>c</sub> is B<sub>c</sub> and is called *susceptance*

So now:  $I = VB_C$ 

#### **ELI the ICE man** (A catchy memorable phrase)

#### **Current leads the voltage in a capacitive circuit.**

# ELI

#### I = Current C = Capacitance E = Voltage

(The hard part is remembering why I=Current and E=Voltage)

# Check Your Knowledge: Fundamentals of Electricity

- With a Voltage of 120 volts, Resistance of 10Ω and Inductive Reactance of 5Ω. What is the current?
- 2. Does the current lead or lag the voltage?
- 3. What is the angle between the current and the voltage legs of the triangle?

# **Power in AC Circuits**

- Resistive Circuits Watts
- Reactive Circuits VARS
- Complex Power
- Power Triangle
- Power Factor
- VARs Effect on Voltage
- Voltage Collapse



# **Power Capacitors**







## **Resistive Circuits - Watts**


WESTERN ELECTRICITY COORDINATING COUNCIL

### Power in AC Circuits Resistive Circuits

*Power* is the rate at which work is performed it is measured in *watts*.

- In a resistive circuit, the current and voltage are in phase.
- *Real Power* is the power consumed by the resistance in a circuit.
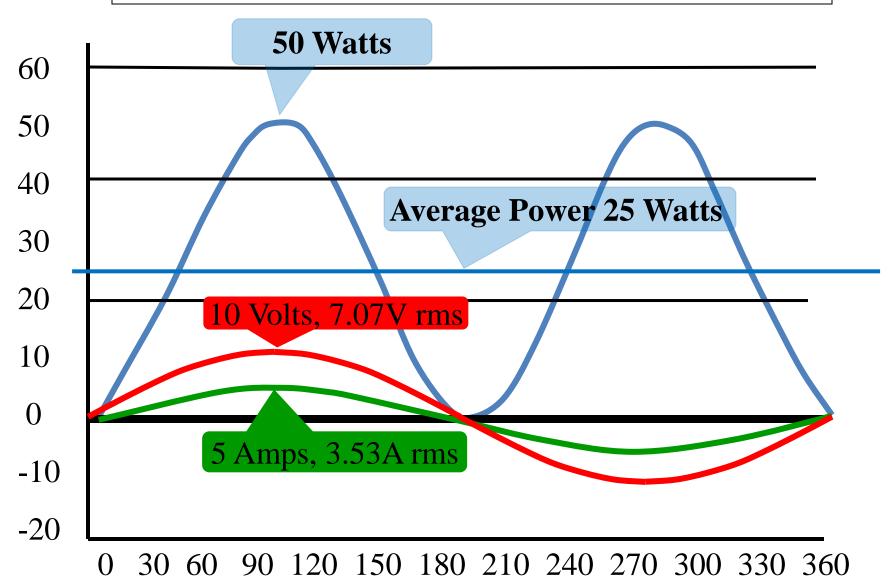
#### **REAL POWER IN A RESISTIVE CIRCUIT**



Power in AC Circuits Resistive Circuits

Real power is calculated using the following equations:

$$P = IV = I(IR) = I^2 R$$
$$P = \frac{VV}{R} = \frac{V^2}{R}$$

## Power in AC Circuits Resistive Circuits


- Losses are dissipated as heat in transmission lines and transformers
- I<sup>2</sup>R = Heating Losses
- Most circuits are not entirely resistive they contain reactance

## **Reactive Circuits - VARs**

WESTERN ELECTRICITY COORDINATING COUNCIL

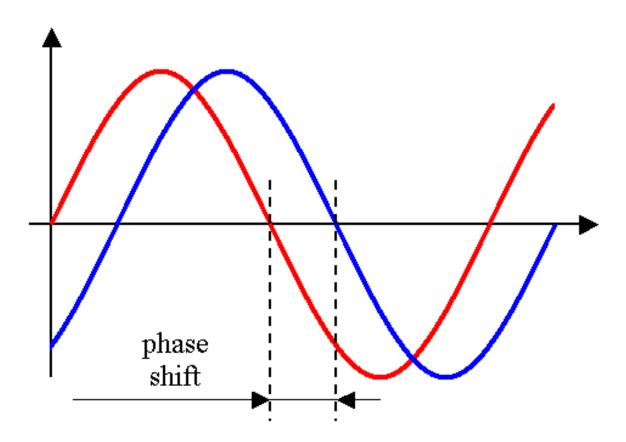
#### Power in AC Circuits Reactive Circuits

Reactance causes a phase shift between voltage and the current.



Power in AC Circuits Reactive Circuits

#### $V = IR + IX < 90^{\circ}$

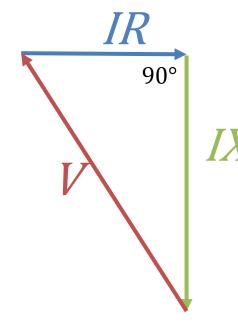

Note: Reactive Impedance of a IX Transmission line is much larger then the resistance.

#### Power in AC Circuits Reactive Circuits

Reactive Power is the power used to support the magnetic and electric fields found in inductive and capacitive loads throughout a power system.

• Reactive power is measured in volt-amps-reactive (Vars)

# **Complex Power**


WESTERN ELECTRICITY COORDINATING COUNCIL


#### **Complex Power = Real Power + Reactive Power**.

- Unlike resistors; inductors and capacitors do not consume power, they store and release energy
- In a resistive circuit, the current and voltage are in phase. But that is not the case in a reactive circuit

- Reactive Power supports the magnetic and electric fields found in inductive and capacitive loads
- Reactive power is measured in voltamperes reactive (Vars)

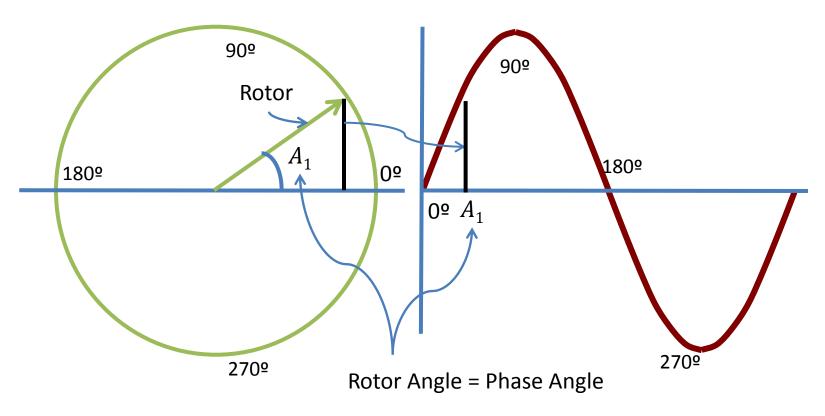We use phasors and **right triangle relationships** to break the current and voltage into resistive and reactive parts.




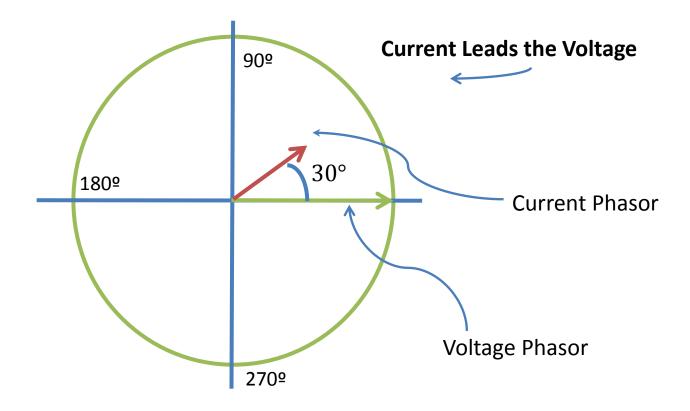

Current leads Voltage by 30<sup>o</sup>

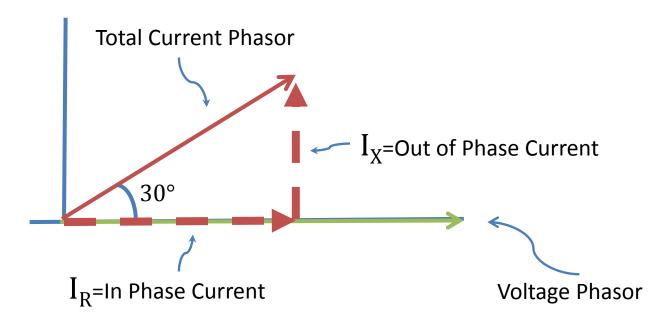
**Capacitive Circuit** 

Part of the Current is in-phase with the voltage. Part of the Current is out-of-phase with the voltage.




Current leads Voltage by 30<sup>o</sup>

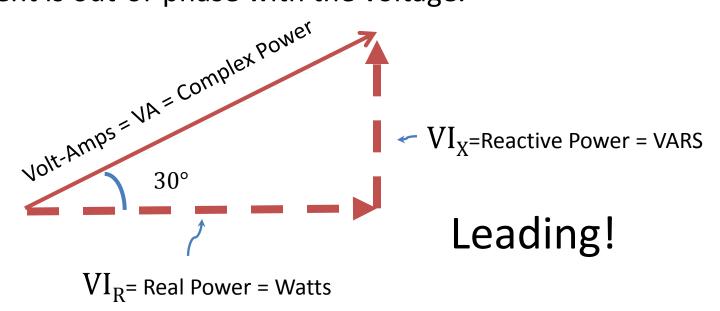Part of the Current is in-phase with the voltage. Part of the Current is out-of-phase with the voltage.



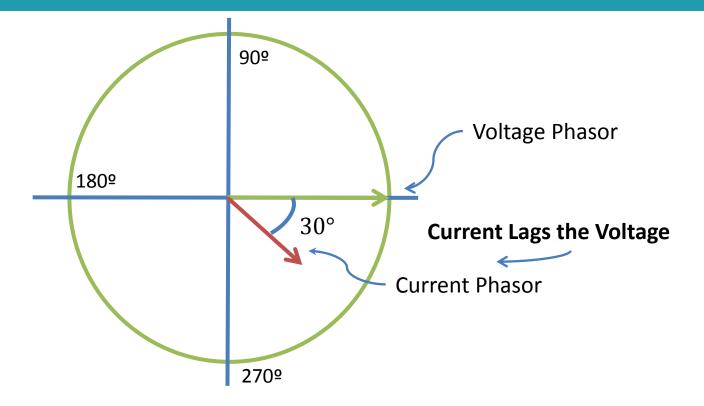
#### Current leads Voltage by 30<sup>o</sup>



Current Lags Voltage by 30<sup>o</sup>

#### **Inductive Circuit**

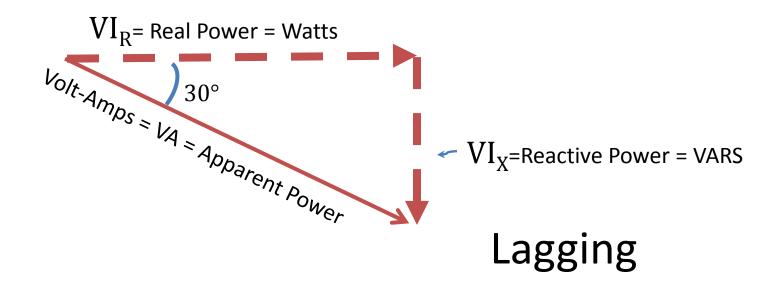

#### **Inductive Circuit**

Current Lags Voltage by 30<sup>o</sup>

- When voltage and current are not in phase or in sync, there are two components:
  - Real or active power is measured in Watts
  - Reactive (sometimes referred to as imaginary) power is measured in VARs
- The combination (vector product) is Complex Power or Apparent Power
- The term "Power" normally refers to active power

**Real power** does the work; it does the heating, lighting, and turning of motors, etc.

It is measured in Watts


**Reactive power** supports magnetic and electric fields required for AC systems to function.

It is measured in:

Volt-Amperes-Reactive (VARs)

# Power Triangle

## Power in AC Circuits Power Triangle

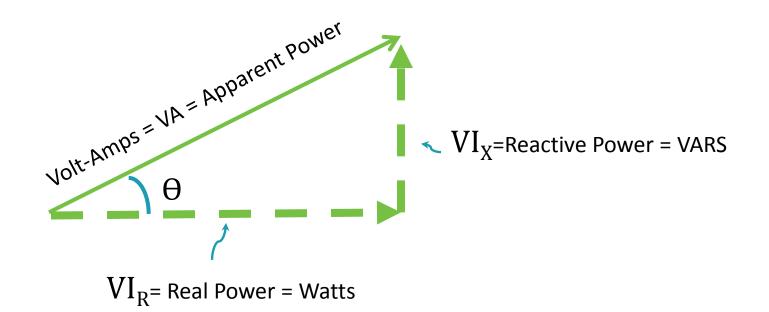

#### Angle between Apparent Power and Real Power is $\boldsymbol{\theta}$


## **Power Factor**

WESTERN ELECTRICITY COORDINATING COUNCIL

**Power Factor (PF)** is the ratio of real power to apparent power.

Power factor =  $\frac{Watts}{VA}$ VA = Apparent Power VARS VA =  $\Theta$  Watts
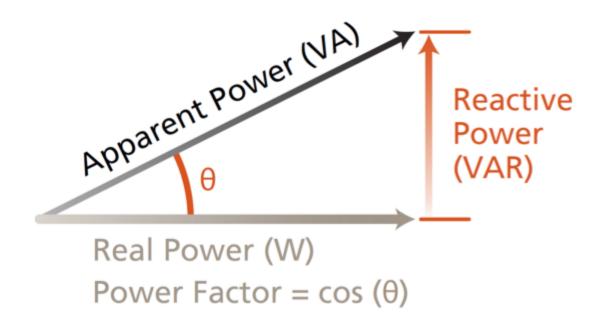
#### The Power Factor ( $\cos \Theta$ ) = Real/Apparent



# To serve Manufacturer A, the utility must provide the following volt-amperes.

$$P_{app} = \frac{P}{PF}$$
  
 $P_{app} = \frac{2,000,000}{.6}$   
 $P_{app} = 3,333,333.3$   
 $P_{app} = 3.3MVA$ 

To serve this load, the utility's conductors must be able to carry the following current:

$$I = \frac{P_{app}}{V}$$

$$I = \frac{3,333,333.3 \text{ VA}}{4,700 \text{ V}}$$

$$I = 709.2 \text{ A}$$

Manufacturer B uses the same real power (2 MW) as Manufacturer A and, therefore, pays the same amount to the utility. However, Manufacturer B requires a different amount of apparent power.

P<sub>app</sub> = 
$$\frac{P}{PF}$$
  
P<sub>app</sub> =  $\frac{2,000,000}{.97}$   
P<sub>app</sub> = 2,061,856 VA  
P<sub>app</sub> = 2,1MVA

And, the current drawn by Manufacturer B is:

$$I = \frac{P_{app}}{V}$$
  
 $I = \frac{2,061,856 \text{ VA}}{4,700 \text{ V}}$ 

I = 439 A

Manufacturer B draws much less current to obtain the same real power.

Utilities design their transmission and distribution systems based on the apparent power and the current they must deliver.

Since utilities bill their customers for the true power used, utilities encourage the use of high-power factor systems.

# VARs – Effect on Voltage

WESTERN ELECTRICITY COORDINATING COUNCIL


## Power in AC Circuits VAR Effect on Voltage Control

Reactive power supply is the most important element in controlling voltage.

# Why?


If I put a lagging reactive current that is 90° out of phase through a reactive line impedance that is 90° out of phase, it results in a 180° voltage drop.
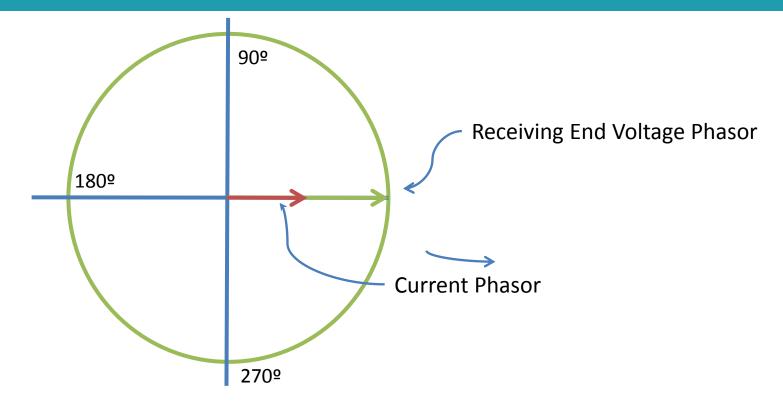
#### Power in AC Circuits VAR effect on Voltage Control




Current In Phase with Voltage

#### **Resistive Load**

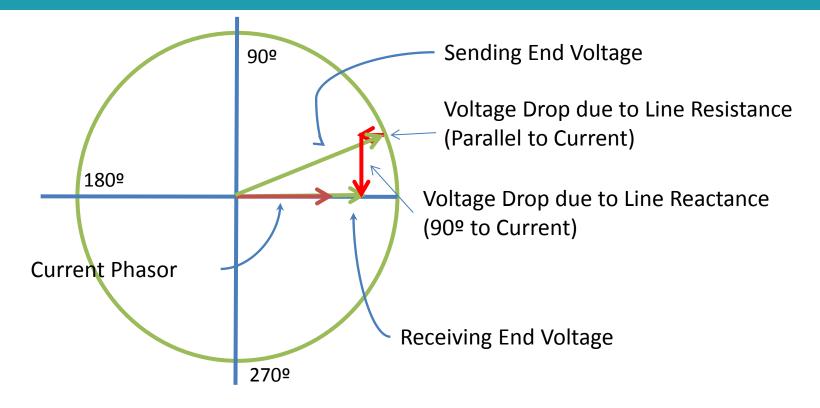


Current In Phase with Voltage

#### **Resistive Load**

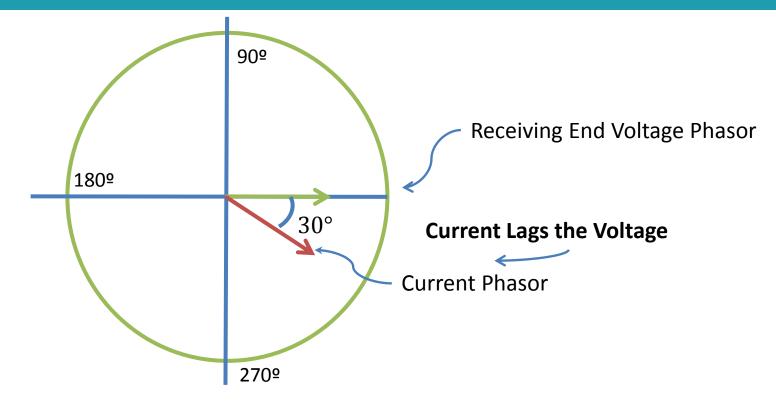


Load Current Lags Voltage by 30<sup>o</sup>

#### **Inductive Load**

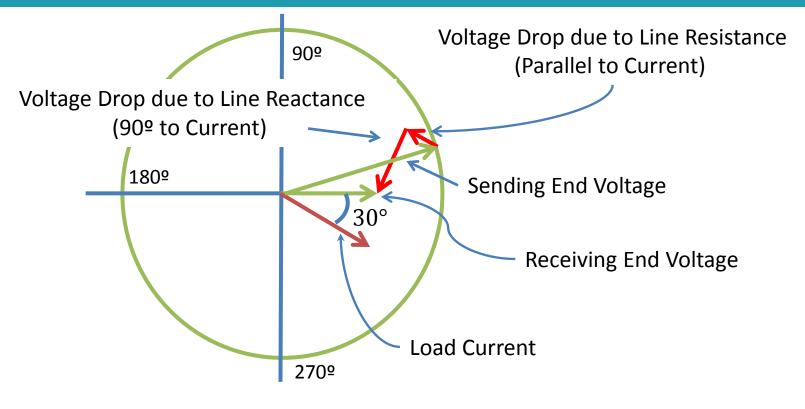

Current Lags Voltage by 30<sup>o</sup>

#### **Inductive Load**

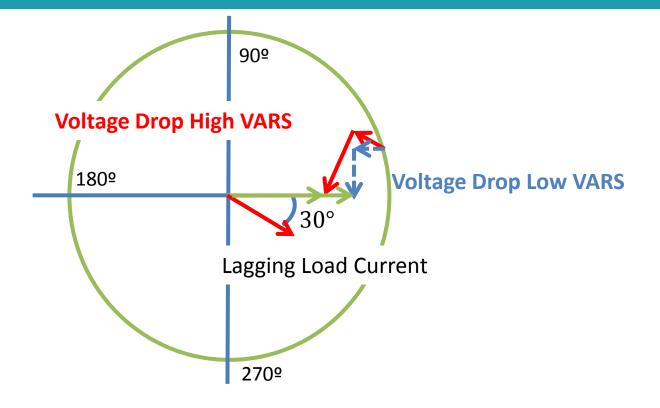

Voltage fluctuates due to:


### Load

- Consumes VARs
- More load, more VARs used
- **Lines** inductive impedance
- More load, more VAR losses
- Loss of a transmission line means other lines load heavier and we experience even more VAR losses
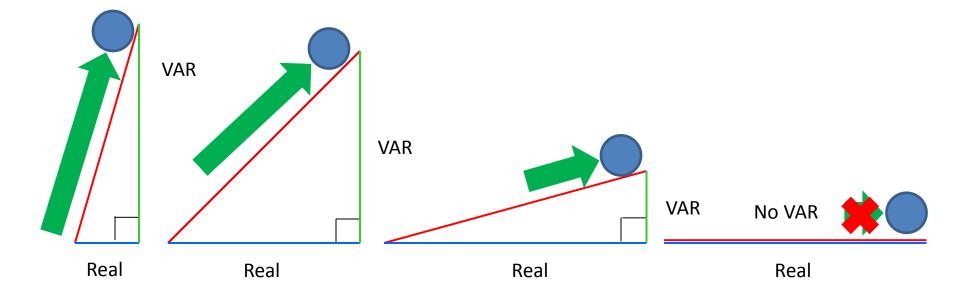
## Voltage Collapse

Power in AC Circuits Voltage Collapse

Voltage Collapse – when the grid system experiences an uncontrollable reduction in voltage due to a deficiency in reactive power (VARS).




### Power in AC Circuits WHAT are VARs?

### **System Operator and Engineering Terms**

- Volt Amp Reactive
- Reactive Power
- Imaginary Power
- Part of Complex Power
- Part of Apparent Power

Power in AC Circuits WHAT are VARs?

#### VAR analogy --- Building a roof

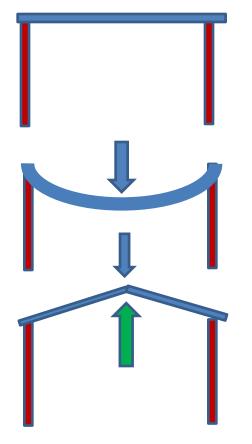

Flat roof with no vertical load is OK (Voltage is OK)

Flat roof with vertical load (VARS) Sags (Voltage Sags)

Slanted roof with VARS added to compensate for load VARS is ok

### Power in AC Circuits WHAT are VARs?

- VARs support the system and pull down or push up the voltage
- When circuits result in the current leading the voltage, voltage rises as VARs increase
- When circuits result in the current lagging the voltage, voltage decreases as VARs are consumed

### Power in AC Circuits Why do WE need Reactive Power

"Reactive power (VARs) is required to maintain the voltage to deliver active power (watts) through transmission lines. Motor loads and other loads require reactive power to convert the flow of electrons into useful work. When there is not enough reactive power, the voltage sags down and it is not possible to push the power demanded by loads through the lines."

("Signatures of the Blackout of 2003", Roger C. Dugan et. al.)

### Power in AC Circuits Importance of Reactive Power

- Refers to the circulating power in the grid that does no useful work
- Results from energy storage elements in the power grid (mainly inductors and capacitors)
- It must be controlled to prevent voltage problems.
- Reactive power levels have an effect on voltage collapse
- The reactive power flow should be minimized to reduce losses. This ensures that the system operates efficiently

### Power in AC Circuits Reactive Power is a Byproduct of AC systems

- Transformers, transmission lines, and motors require reactive power.
- Transformers and transmission lines introduce inductance as well as resistance.

#### • Both oppose the flow of current

• Must raise the voltage higher to push the power through the inductance of the lines.


#### • Unless capacitance is introduced to offset inductance


• The farther the transmission of power, the higher the voltage needs to be raised.

### Power in AC Circuits Reactive Power & Power Factor

- Reactive power is present when the voltage and current are not in phase
  - One waveform leads the other
  - Phase angle not equal to Zero Degrees
  - Power factor less than unity
- Measured in volt-ampere reactive (VAR)
- Produced when the current waveform leads voltage waveform (Leading power factor)
- Vice versa, consumed when the current waveform lags voltage (lagging power factor)
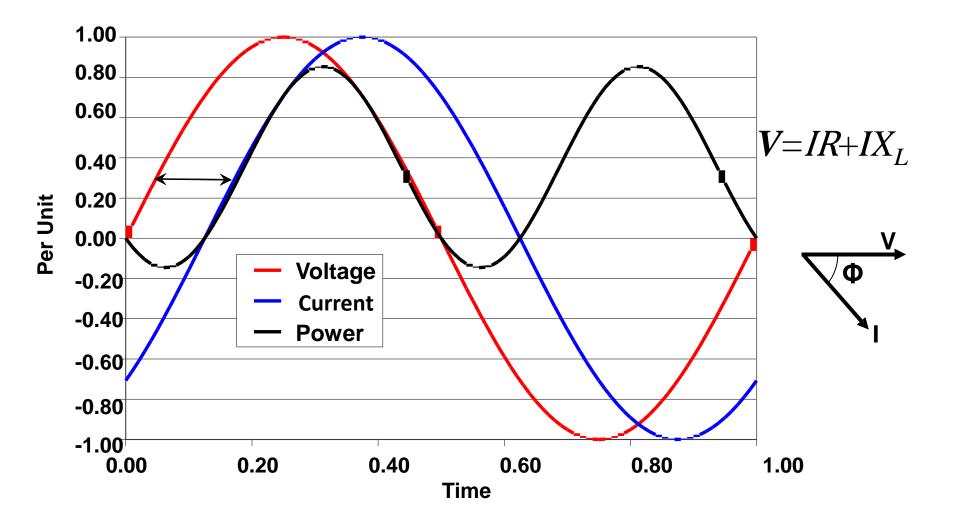
### AC Voltage & Current Phase Shift due to Inductance Current Lags Voltage



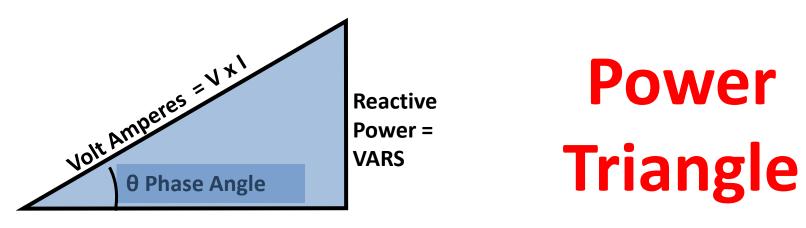

True Power = Watts

Volt-Amperes = (VA) = Apparent Power

Watts = (W) = True Power


Vars = (VARS) = Volt-Amperes Reactive

Power Factor = (PF) = Watts/(Volt Amperes)

Phase Angle =  $\Theta$  = COS<sup>-1</sup> (PF) = Angular displacement between voltage & current Power in AC Circuits Power Triangle

Complex Power =  $\sqrt{(\text{Real Power})^2 + (\text{Reactive Power})^2}$ 

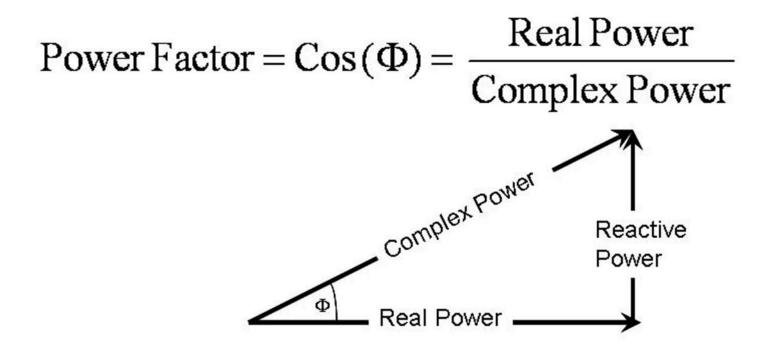Real Power = Complex Power  $\times$  Cos( $\Phi$ )



### Power in AC Circuits Reactive Power Limitations

- Reactive power does not travel very far
- Usually necessary to produce it close to the location where it is needed
- A supplier/source close to the location of the need is in a much better position to provide reactive power

versus one that is located far from the location of the need

 Reactive power supplies are closely tied to the ability to deliver real or active power

# Check Your Knowledge: Fundamentals of Electricity

- In a Resistive Load the current A) Leads, B) Lags,
   C) is in phase with the voltage. T/F?
- 2. A load consists of a 4 ohms resistor in parallel with a 3 ohm reactor with a voltage of 10 volts.
  - a. What is the total Impedance?
  - b. Current?
  - c. Real Power?
  - d. Reactive Power?
  - e. Power Factor?

## **Three-Phase Circuits**


- Definition and Advantages
- Three Phase Connections


# WYE vs. Delta

WESTERN ELECTRICITY COORDINATING COUNCIL

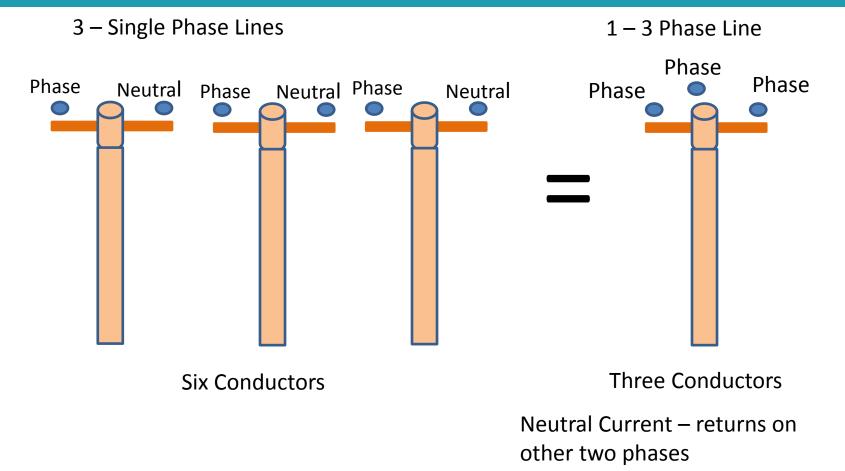
### **Definition and Advantages**

- Almost all electricity is generated and distributed as *three-phase* rather than singlephase
- Cost of three-phase is less than single-phase
- Uses fewer conductors
- Reduces Losses



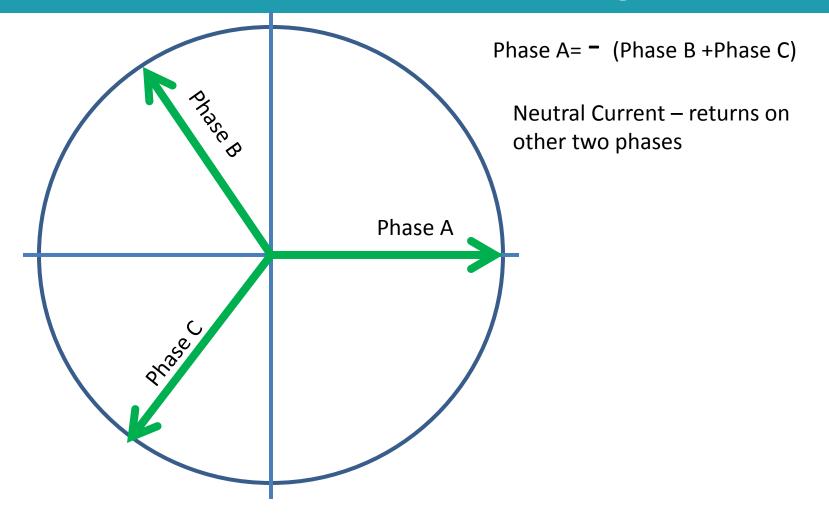

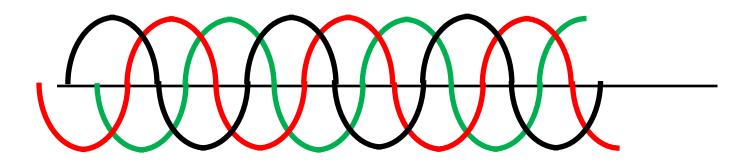- More constant load on the generator shaft.
- Single-phase load on the generator shaft goes from zero to maximum power and back to zero with each cycle.
- With three-phase current, at least two of the phases provide current (and therefore, power) at any instant.
- Load on a three-phase generator never reduces to zero. This uniform load allows smoother operation of the generator...




### A Phase B Phase C Phase

In a three-phase circuit:


- An AC voltage generator produces three evenly spaced sinusoidal voltages, identical except for a phase angle difference of 120<sup>o</sup>
- Three conductors transmit the electric energy. The conductors are called phases and are commonly labeled A Phase, B Phase, and C Phase
- Each phase conductor carries its own phase current
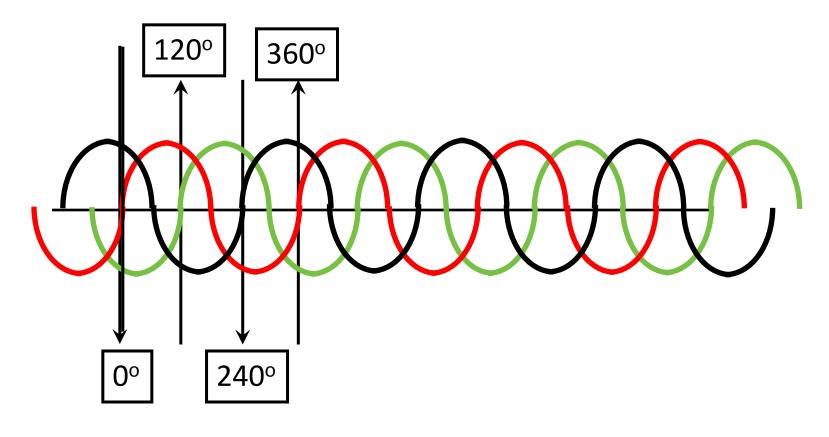
### Three-Phase Circuits Three-Phase Power




A Phase B Phase C Phase

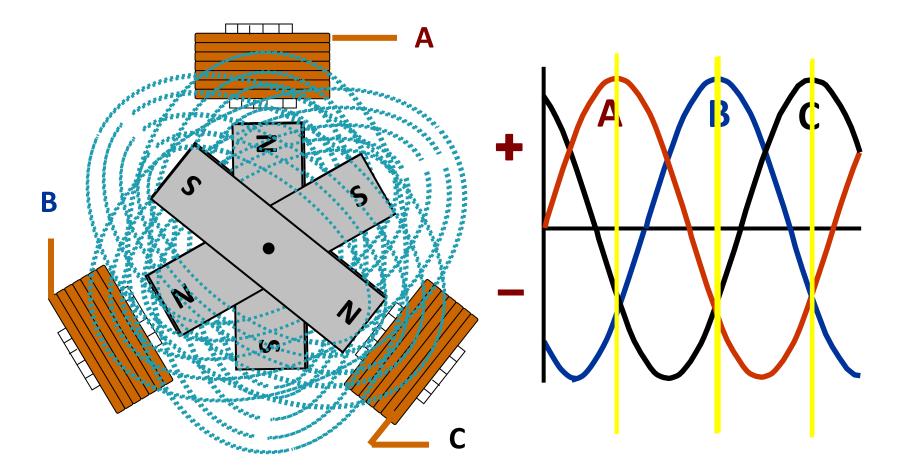
### Three-Phase Circuits Generating 3-Phase Power Waves


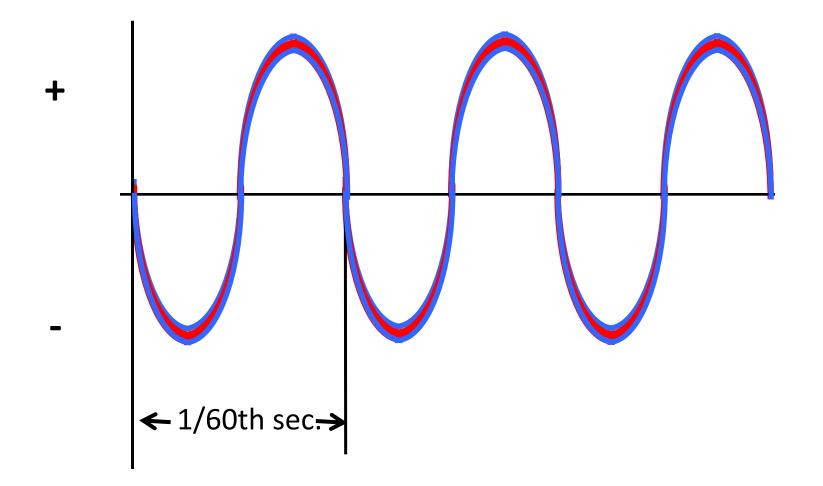
### Three-Phase Circuits vs. Single Phase Power


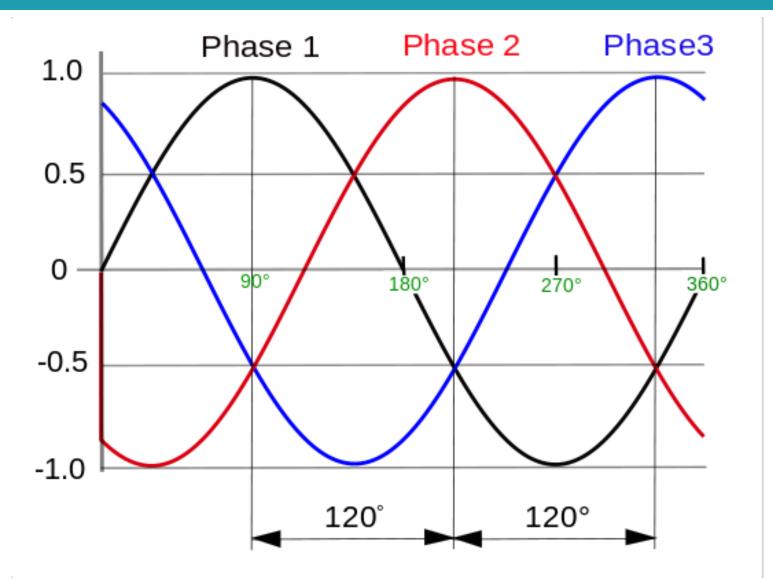
### Three-Phase Circuits Three-Phase Power



### Three-Phase Circuits Interconnected 3-Phase Power

In an AC interconnection, all connected utilities see the same electrical frequency and all generators operate in synchronism with each other.




- Definition: Phase-to-Phase and Line Voltages
- The voltages between the outputs of the generator are called the *line voltages* (sometimes called phase-to-phase voltages).
- The line voltages are equal to the phase voltages.
- When a Delta-connected generator is loaded, current flows in the loads, lines, and phase windings.


### **Three-Phase Circuits**

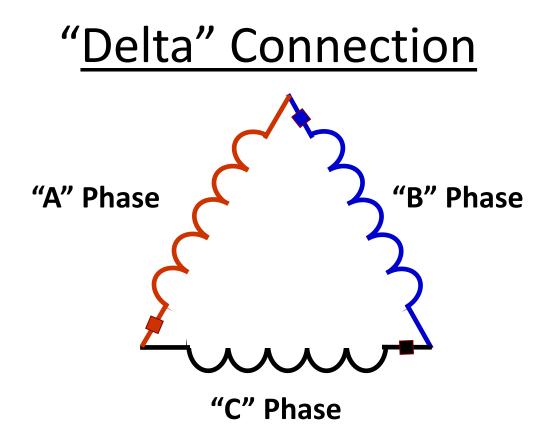
### Three-Phase Circuits Three Phase Connections

The line currents are not equal to the phase currents, because each line carries current from two phases. The currents from any two phases are 120° out of phase.


 $I_{line} = \sqrt{3} I_{phase}$  $I_{line} = 1.732 I_{phase}$ ( $\sqrt{3}$  is approximately 1.732)



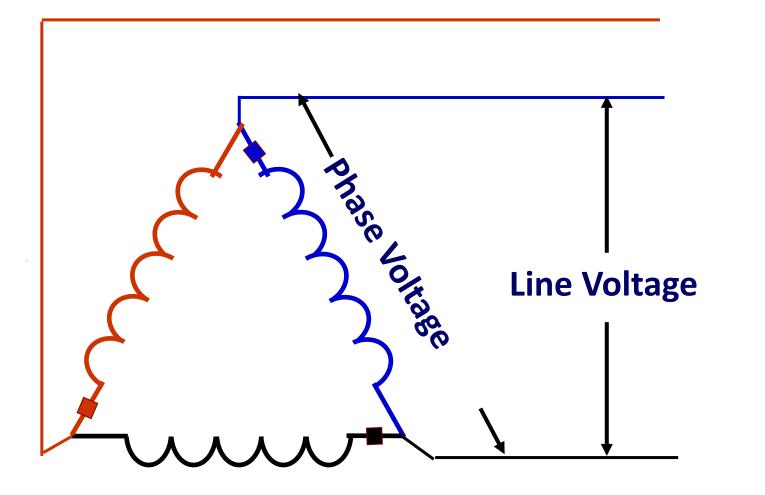


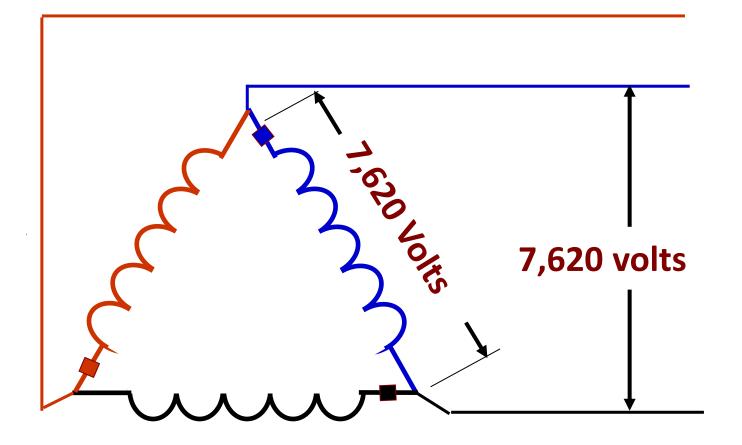



**Phase Voltage = Line Voltage** 

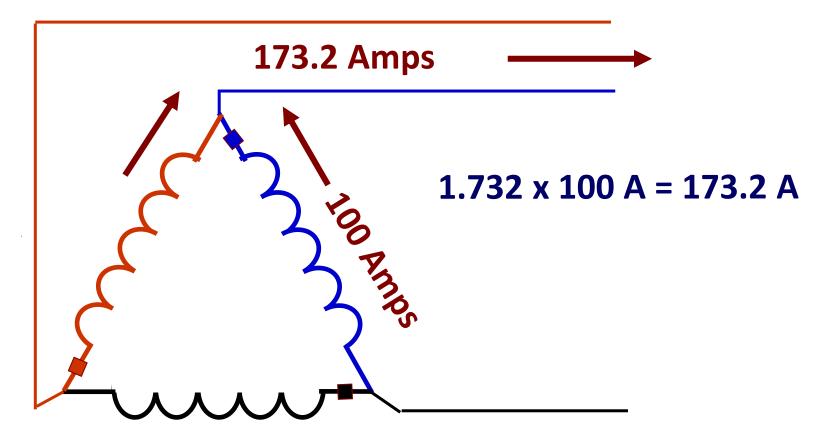


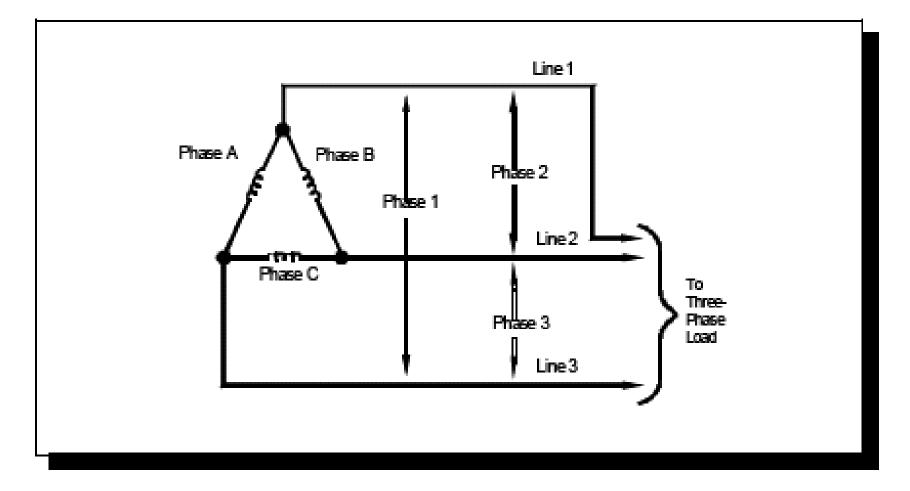
Line Current = Phase Current x  $\sqrt{3}$  = PC x 1.732



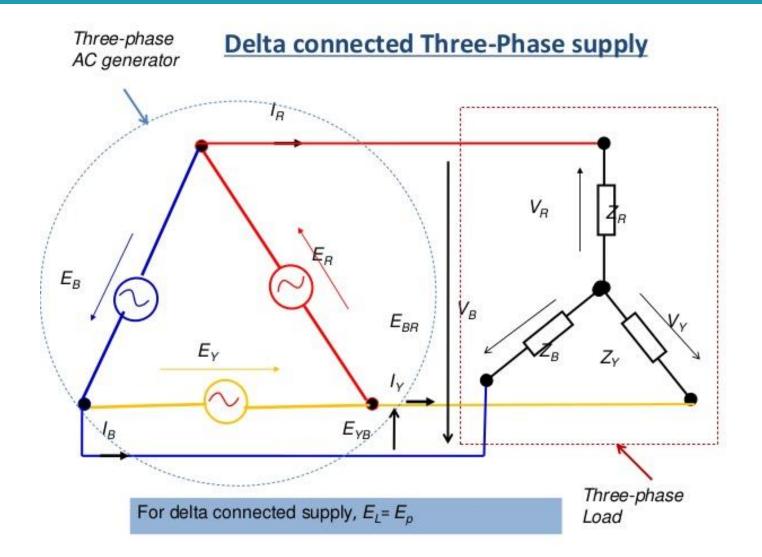


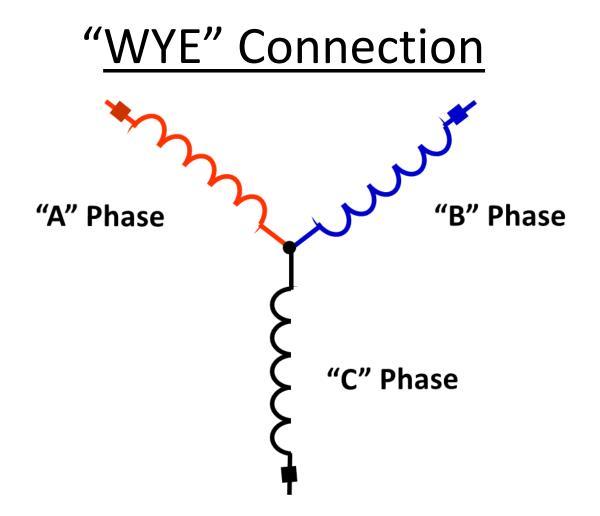

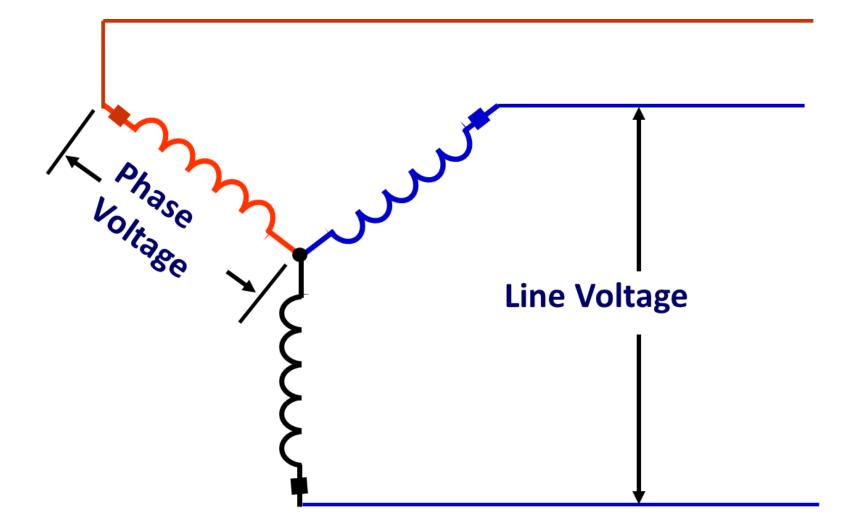


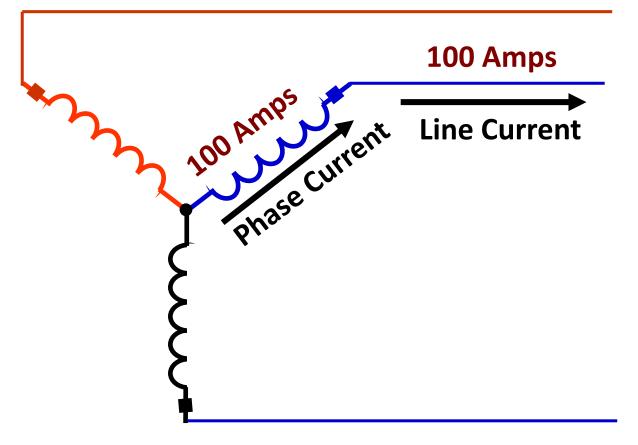

#### **Phase Current = Line Current**

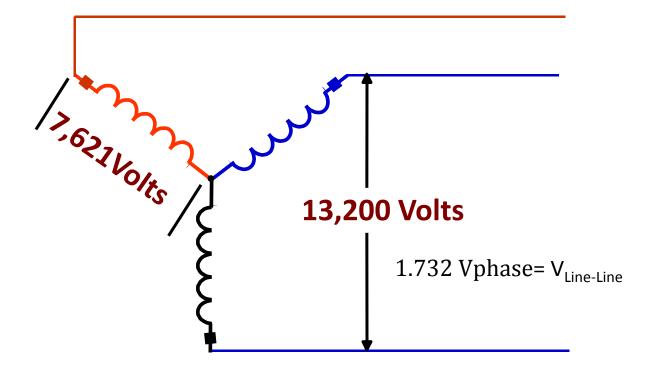

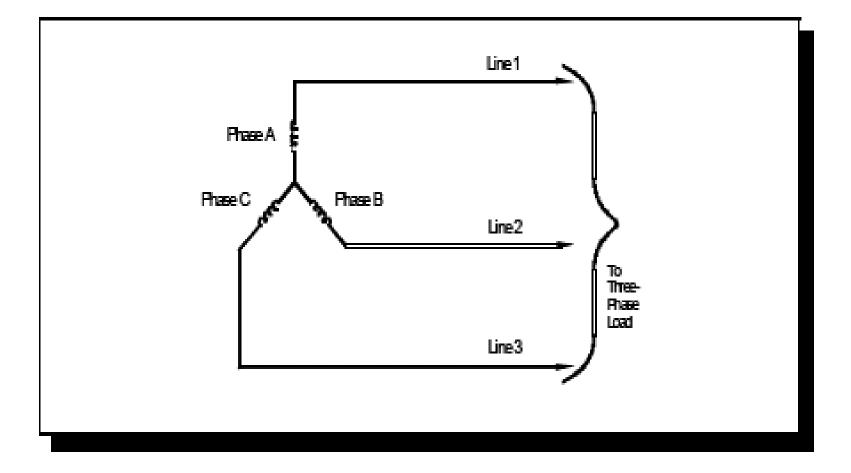Line Voltage = Phase Voltage x  $\sqrt{3}$  = PV x 1.732



## Electromechanics


- Definition
- Generators
- Motors
- Synchronous Condenser

#### Electromechanics Definition

**Electromechanical Energy Conversion** is used by generators and motors.


 This process transforms mechanical energy into electrical energy and vice versa Electromechanics Generators

#### A simple Generator

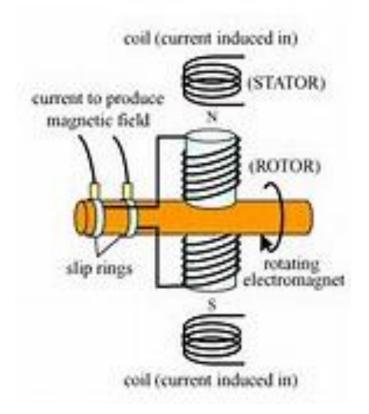

Electromechanics Motors

#### **A simple Motor**

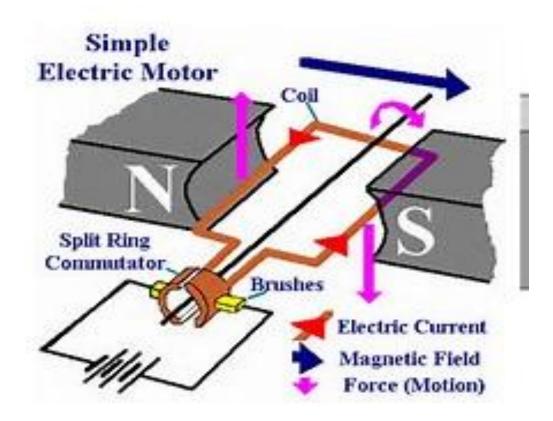

## **Generators and Motors**


#### Electromechanics Generators and Motors

A *generator* converts mechanical energy into electrical energy.


 A voltage is induced in stator conductors as the magnetic flux from the rotor moves past them

A *motor* converts electrical energy into rotary motion.

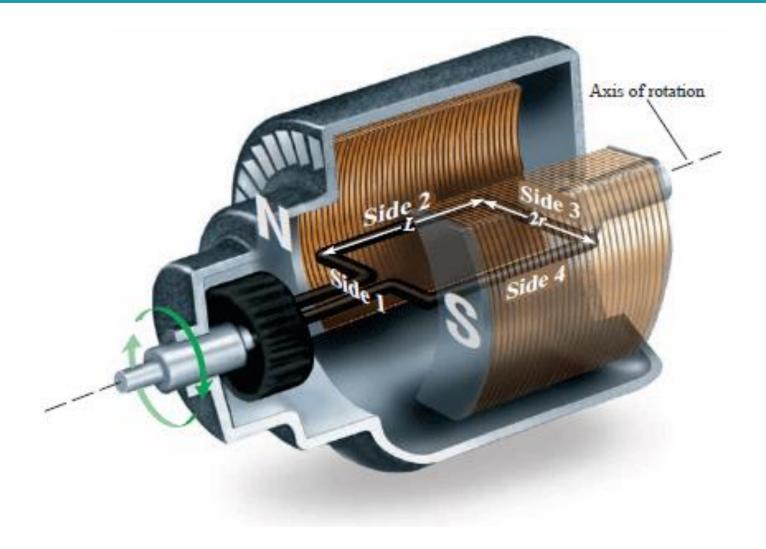
 Current-carrying conductors in the rotor experience a force at right angles to the magnetic field of the motor Electromechanics Generators



### Electromechanics Generators

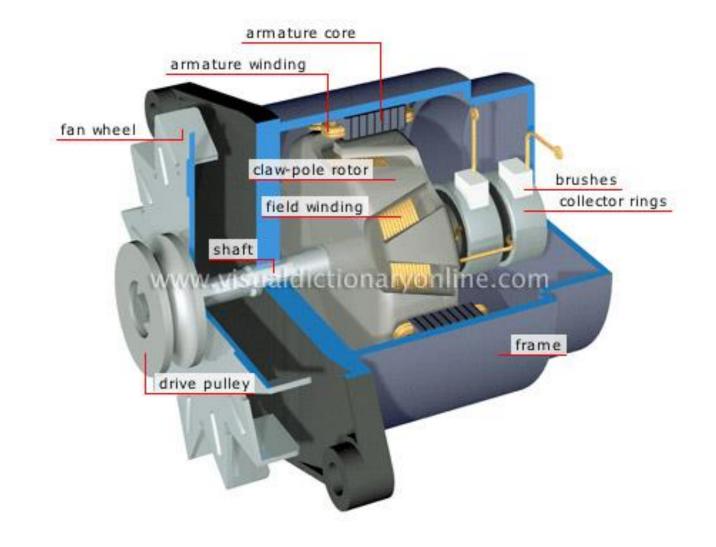

### Electromechanics Motors

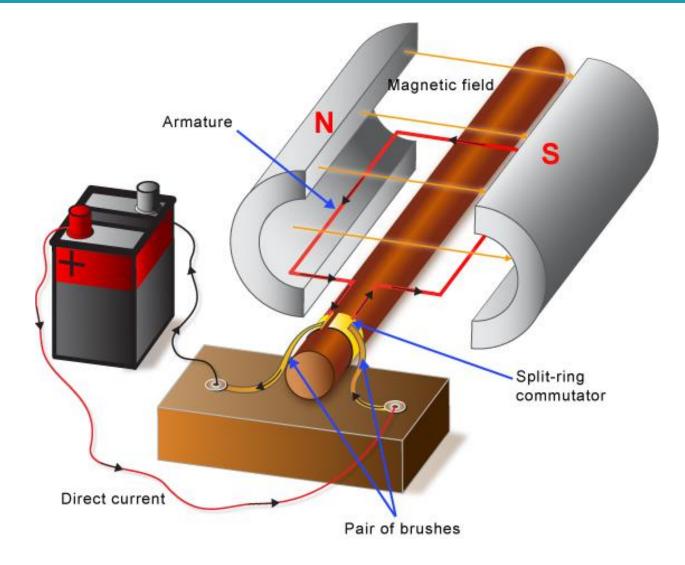

# Sychronous Condenser

### Electromechanics Synchronous Condenser

A *synchronous condenser* is a large synchronous motor.

- A synchronous condenser is used to generate or absorb VARs
- Operators can control whether it produces or consumes VARs

# Check Your Knowledge: Fundamentals of Electricity

- 1. A conductor is a material that has only a few free valance electrons that continually jump to other atoms. T/F?
- 2. What are two materials that are good electrical conductors?
- 3. An insulator is a material that has a large number of free valance electrons that continually jump to other atoms. T/F?
- 4. What are two materials that are good electrical insulators.
- 5. Whenever current flows in a conductor, what invisible force surrounds the conductor?
- 6. In an inductive circuit, does the current *lead or lag* the voltage?
- 7. What is impedance?